
DIGITAL DESIGN

Through Embedded Programming

G. V. V. Sharma



Copyright ©2022 by G. V. V. Sharma.

<https://creativecommons.org/licenses/by-sa/3.0/>

and

<https://www.gnu.org/licenses/fdl-1.3.en.html>

Contents

Introduction	iii
1 Installation	1
1.1 Termux	1
1.2 Platformio	2
1.3 Arduino Droid	3
2 Seven Segment Display	5
2.1 Components	5
2.1.1 Breadboard	5
2.1.2 Seven Segment Display	6
2.1.3 Arduino	6
2.2 Display Control through Hardware	6
2.2.1 Powering the Display	6
2.2.2 Controlling the Display	7
2.3 Display Control through Software	8
3 7447	11
3.1 Components	11
3.2 Hardware	11

3.3	Software	12
3.4	Problems	14
4	Karnaugh Map	45
4.1	Introduction	45
4.2	Incrementing Decoder	45
4.3	Karnaugh Map	45
4.4	Dont Care	50
4.5	Don't Care Conditions	51
4.6	Problems	54
5	7474	87
5.1	Components	87
5.2	Decade Counter	87
5.3	Problems	89
6	Finite State Machine	109
6.1	The Decade Counter	109
6.2	Finite State Machine	109
6.3	Problems	110

Introduction

This book introduces digital design through using the arduino framework.

Chapter 1

Installation

1.1. Termux

1. On your android device, install fdroid apk from

```
https://www.f-droid.org/
```

2. Install Termux from apkpure
3. Install basic packages on termux

```
#Give termux access to your user directory in android
termux-setup-storage

#Upgrade packages
apt update && apt upgrade
apt install build-essential openssh

#Mandatory packages
apt install curl git wget subversion proot proot-distro python nmap neovim ranger
#-----End Install Termux
```



```
-----
```

4. Install Ubuntu on termux

```
proot-distro install ubuntu
proot-distro login ubuntu
```

1.2. Platformio

1. Install Packages

```
apt update && apt upgrade
apt install apt-utils build-essential cmake neovim
apt install git wget subversion imagemagick nano
apt install avra avrdude gcc-avr avr-libc
#-----End Installing ubuntu on termux
-----

#----- Installing python3 on termuxubuntu
-----

apt install python3-pip python3-numpy python3-scipy python3-matplotlib
python3-mpmath python3-sympy python3-cvxopt
#----- End installing python3 on termuxubuntu
-----

#----- Installing platformio on termuxubuntu
```

```
python3 -m venv gvenv
source gvenv/bin/activate
pip3 install platformio
#----- End installing python3 on termuxubuntu
```

2. Execute the following on ubuntu

```
cd ide/piosetup/codes
pio run
```

3. Connect your arduino to the laptop/rpi and type

```
pio run -t nobuild -t upload
```

4. The LED beside pin 13 will start blinking

1.3. Arduino Droid

1. Install ArduinoDroid from apkpure
2. Open ArduinoDroid and grant all permissions
3. Connect the Arduino to your phone via USB-OTG
4. For flashing the bin files, in ArduinoDroid,

```
Actions->Upload->Upload Precompiled
```

then go to your working directory and select

```
pio/build/uno/firmwarehex
```

for uploading hex file to the Arduino Uno

5. The LED beside pin 13 will start blinking

Chapter 2

Seven Segment Display

We show how to control a seven segment display.

2.1. Components

Component	Value	Quantity
Breadboard		1
Resistor	$\geq 220\Omega$	1
Arduino	Uno	1
Seven Segment Display	Common Anode	1
Jumper Wires		20

Table 2.1:

2.1.1. Breadboard

The breadboard can be divided into 5 segments. In each of the green segments, the pins are internally connected so as to have the same voltage. Similarly, in the central segments, the pins in each column are internally connected in the same fashion as the blue columns.

2.1.2. Seven Segment Display

The seven segment display in Fig. 2.2 has eight pins, a, b, c, d, e, f, g and dot that take an active LOW input, i.e. the LED will glow only if the input is connected to ground. Each of these pins is connected to an LED segment. The dot pin is reserved for the \cdot LED.

2.1.3. Arduino

The Arduino Uno has some ground pins, analog input pins A0-A3 and digital pins D1-D13 that can be used for both input as well as output. It also has two power pins that can generate 3.3V and 5V. In the following exercises, only the GND, 5V and digital pins will be used.

2.2. Display Control through Hardware

2.2.1. Powering the Display

1. Plug the display to the breadboard in Fig. 2.1 and make the connections in Table 2.2.

Henceforth, all 5V and GND connections will be made from the breadboard.

Arduino	Breadboard
5V	Top Green
GND	Bottom Green

Table 2.2: Supply for Bread board

2. Make the connections in Table 2.3.
3. Connect the Arduino to the computer. The DOT led should glow.

 


Figure 2.1: Bread board connections

Breadboard		Display
5V	Resistor	COM
GND		DOT

Table 2.3: Connecting Seven segment display on Bread board

2.2.2. Controlling the Display

Fig. 2.3 explains how to get decimal digits using the seven segment display. GND=0.

1. Generate the number 1 on the display by connecting only the pins *b* and *c* to GND (=0). This corresponds to the first row of 2.4. 1 means not connecting to GND.
2. Repeat the above exercise to generate the number 2 on the display.
3. Draw the numbers 0-9 as in Fig. 2.3 and complete Table 2.4

a	b	c	d	e	f	g	decimal
0	0	0	0	0	0	1	0

Table 2.4:

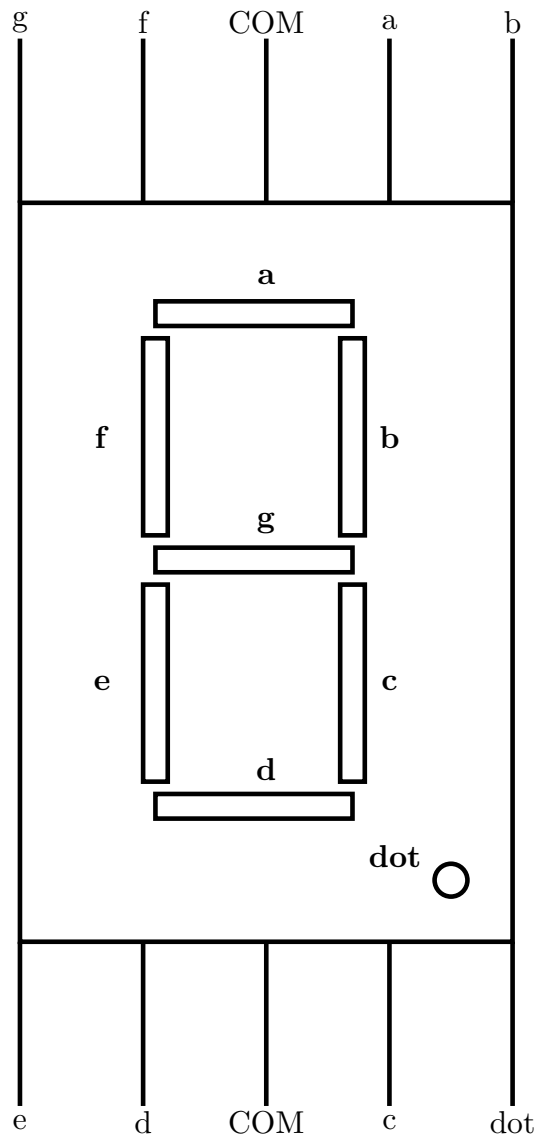


Figure 2.2: Seven Segment pins

2.3. Display Control through Software

1. Make connections according to Table 2.5

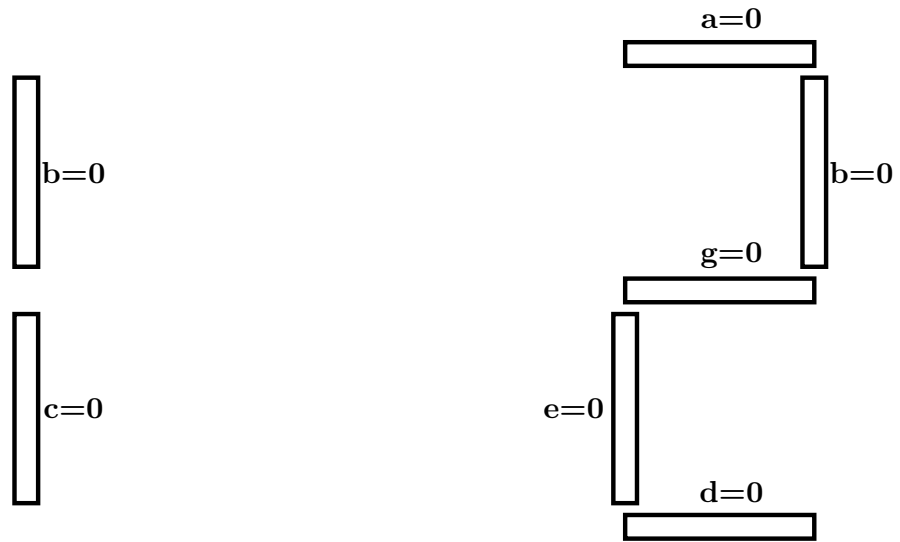


Figure 2.3: Seven Segment connections

Arduino	2	3	4	5	6	7	8
Display	a	b	c	d	e	f	g

Table 2.5:

2. Download the following code using the arduino IDE and execute

```
ide/sevensseg/codes/sevensseg/sevensseg.ino
```

3. Now generate the numbers 0-9 by modifying the above program.

Chapter 3

7447

Here we show how to use the 7447 BCD-Seven Segment Display decoder to learn Boolean logic.

3.1. Components

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Seven Segment Display		1
Decoder	7447	1
Jumper Wires	M-M	20
Breadboard		1

Table 3.1:

3.2. Hardware

1. Make connections between the seven segment display in Fig. 2.2 and the 7447 IC in Fig. 3.1 as shown in Table 3.2

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Table 3.2:

2. Make connections to the lower pins of the 7447 according to Table 3.3 and connect $V_{CC} = 5V$. You should see the number 0 displayed for 0000 and 1 for 0001.

D	C	B	A	Decimal
0	0	0	0	0
0	0	0	1	1

Table 3.3:

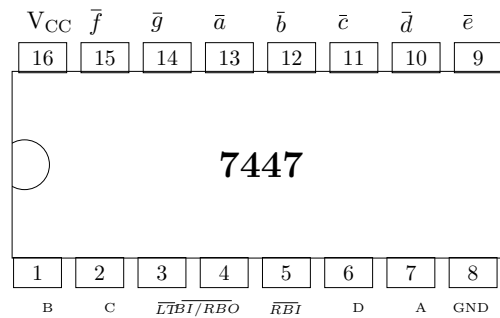


Figure 3.1:

3. Complete Table 3.3 by generating all numbers between 0-9.

3.3. Software

1. Now make the connections as per Table 3.4 and execute the following program

```
ide/7447/codes/gvv_ard_7447/gvv_ard_7447.cpp
```

7447	D	C	B	A
Arduino	5	4	3	2

Table 3.4:

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

Table 3.5: Truth table for incrementing Decoder.

In the truth table in Table 3.5, W, X, Y, Z are the inputs and A, B, C, D are the outputs. This table represents the system that increments the numbers 0-8 by 1 and resets the number 9 to 0. Note that $D = 1$ for the inputs 0111 and 1000. Using boolean logic,

$$D = WXYZ' + W'X'Y'Z \quad (3.1)$$

Note that 0111 results in the expression $WXYZ'$ and 1000 yields $W'X'Y'Z$.

2. The code below realizes the Boolean logic for B, C and D in Table 3.5. Write the logic for A and verify.

```
ide/7447/codes/inc_dec/inc_dec.ino
```

3. Now make additional connections as shown in Table 3.6 and execute the following code. Comment.

```
ide/7447/codes/ip_inc_dec/ip_inc_dec.cpp
```

Solution: In this exercise, we are taking the number 5 as input to the arduino and displaying it on the seven segment display using the 7447 IC.


	Z	Y	X	W
Input	0	1	0	1
Arduino	9	8	7	6

Table 3.6:

4. Verify the above code for all inputs from 0-9.
5. Now write a program where
 - (a) the binary inputs are given by connecting to 0 and 1 on the breadboard
 - (b) incremented by 1 using Table 3.5 and
 - (c) the incremented value is displayed on the seven segment display.
6. Write the truth table for the 7447 IC and obtain the corresponding boolean logic equations.
7. Implement the 7447 logic in the arduino. Verify that your arduino now behaves like the 7447 IC.

3.4. Problems

 1. Obtain the Boolean Expression for the Logic circuit shown below (CBSE 2013)



2. Verify the Boolean Expression (CBSE 2013)

$$A + C = A + A'C + BC \quad (3.2)$$

3. Draw the Logic Circuit for the following Boolean Expression (CBSE 2015)

$$f(x, y, z, w) = (x' + y)z + w' \quad (3.3)$$

4. Verify the following (CBSE 2015)

$$U' + V = U'V' + U'V + UV \quad (3.4)$$

5. Draw the Logic Circuit for the given Boolean Expression (CBSE 2015)

$$(U + V')W' + Z \quad (3.5)$$

6. Verify the following using Boolean Laws (CBSE 2015)

$$X + Y' = XY + XY' + X'Y' \quad (3.6)$$

7. Write the Boolean Expression for the result of the Logic Circuit as shown in Fig. 3.2

(CBSE 2016)

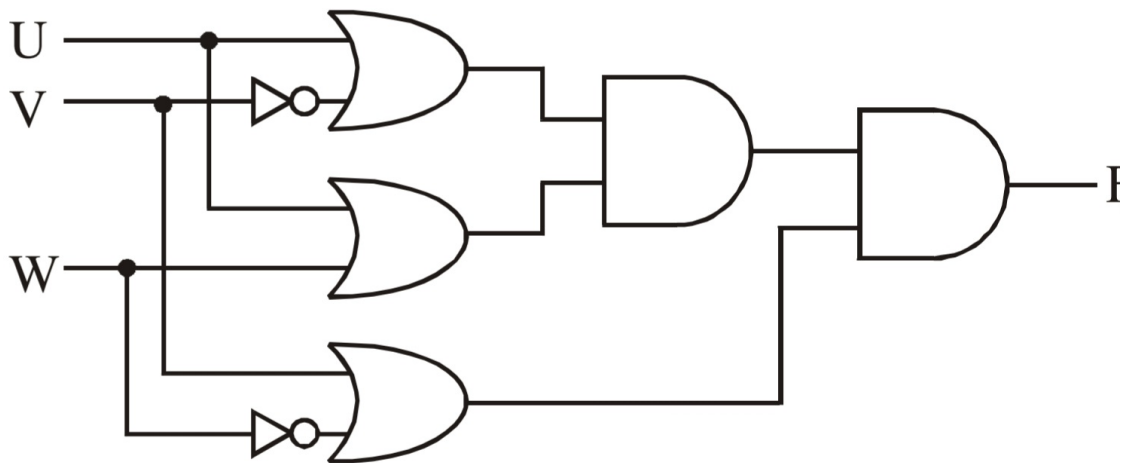


Figure 3.2:

8. Draw the logic circuit of the following Boolean Expression using only NAND Gates.
(CBSE 2017)

$$XY + YZ \quad (3.7)$$

9. Draw the Logic Circuit of the following Boolean Expression using only NOR Gates
(CBSE 2017)

$$(A + B)(C + D) \quad (3.8)$$

10. Draw the Logic Circuit of the following Boolean Expression (CBSE 2018)

$$(U' + V)(V' + W') \quad (3.9)$$

11. Derive a Canonical POS expression for a Boolean function F , represented by Table 3.7 (CBSE 2019)

X	Y	Z	$F(X,Y,Z)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Table 3.7:

12. For the logic circuit shown in Fig.3.3, find the simplified Boolean expression for the output. (GATE EC 2000)


 


Figure 3.3:

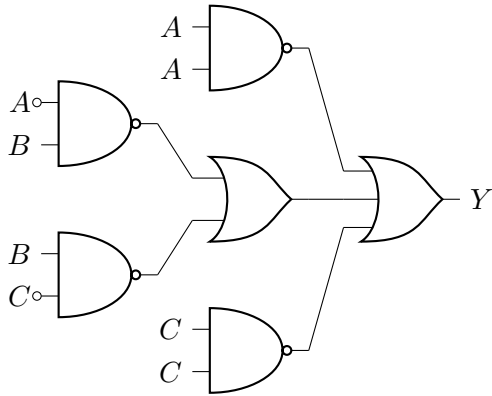13. Obtain the Boolean Expression for the Logic circuit shown below (GATE EC 1993)



14. Implement Table 3.8 using XNOR logic.

(GATE EC 1993)

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Table 3.8:

15. For a binary half-sub-tractor having two inputs A and B, find the correct set of logical expressions for the outputs D (=A minus B) and X (=borrow). (GATE EC 1999)

16. Find X in the following circuit in Fig. 3.4

(GATE EC 2007)

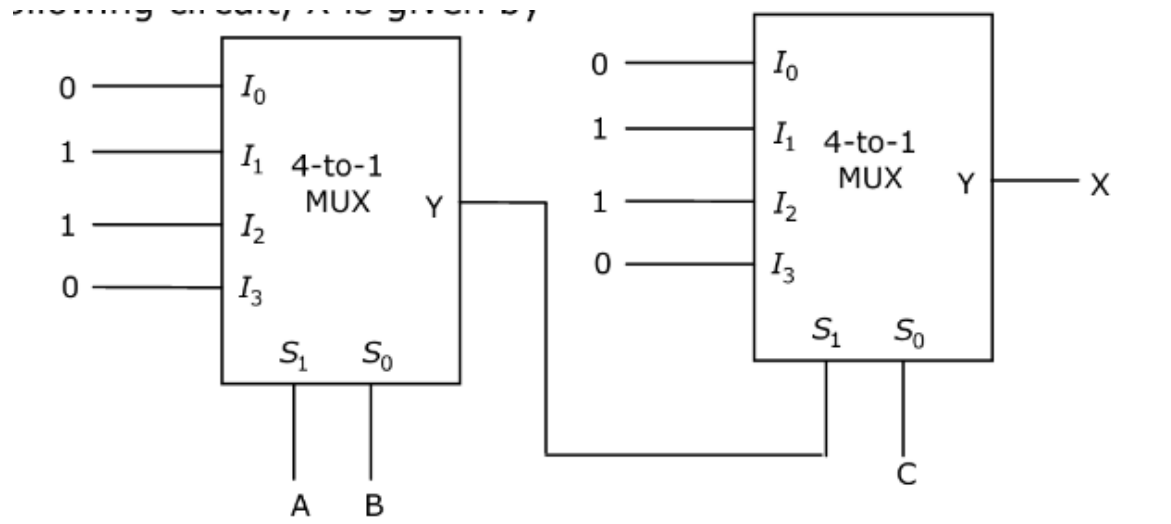


Figure 3.4:

17. A logic circuit implements the boolean function $F = X' \cdot Y + X \cdot Y' \cdot Z'$. It is found that the input combination $X=Y=1$ can never occur. Taking this into account, find a simplified expression for F . (GATE IN 2007)

18. Find the Boolean logic realised by the following circuit in Fig. 3.5 (GATE EC 2010)

 


Figure 3.5:

19. Find the logic function implemented by the circuit given below in Fig. 3.6 (GATE EC 2011)

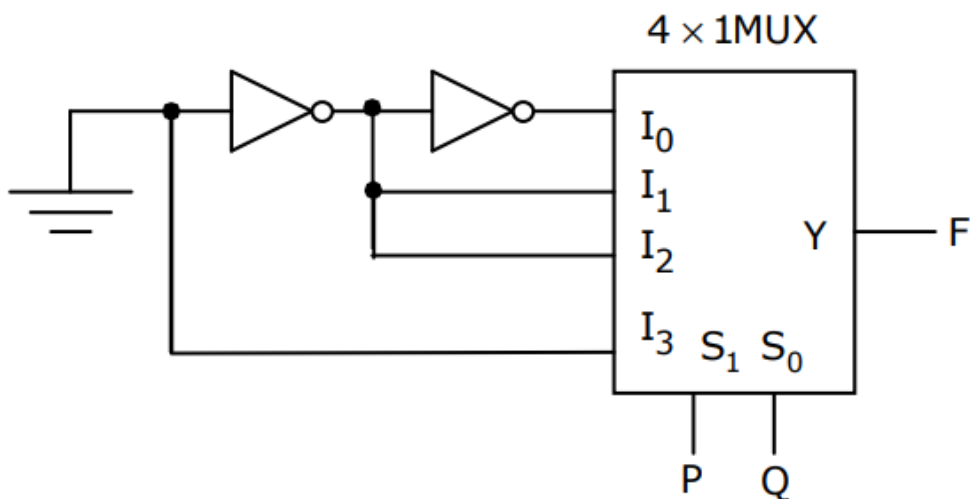


Figure 3.6:

20. Find F in the Digital Circuit given in the figure below in Fig. 3.7. (GATE IN 2016)

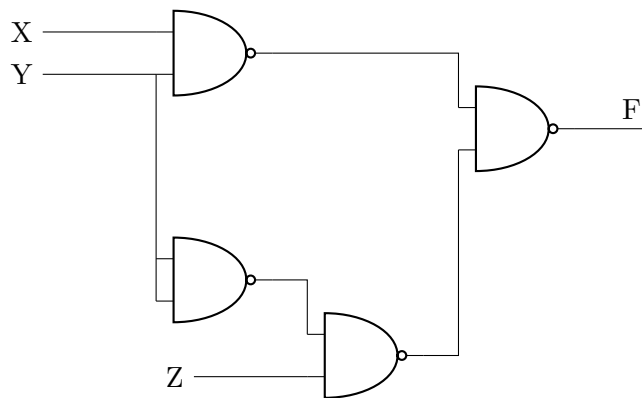


Figure 3.7:

21. Find the logic function implemented by the circuit given below in Fig. 3.8 (GATE EC 2017)

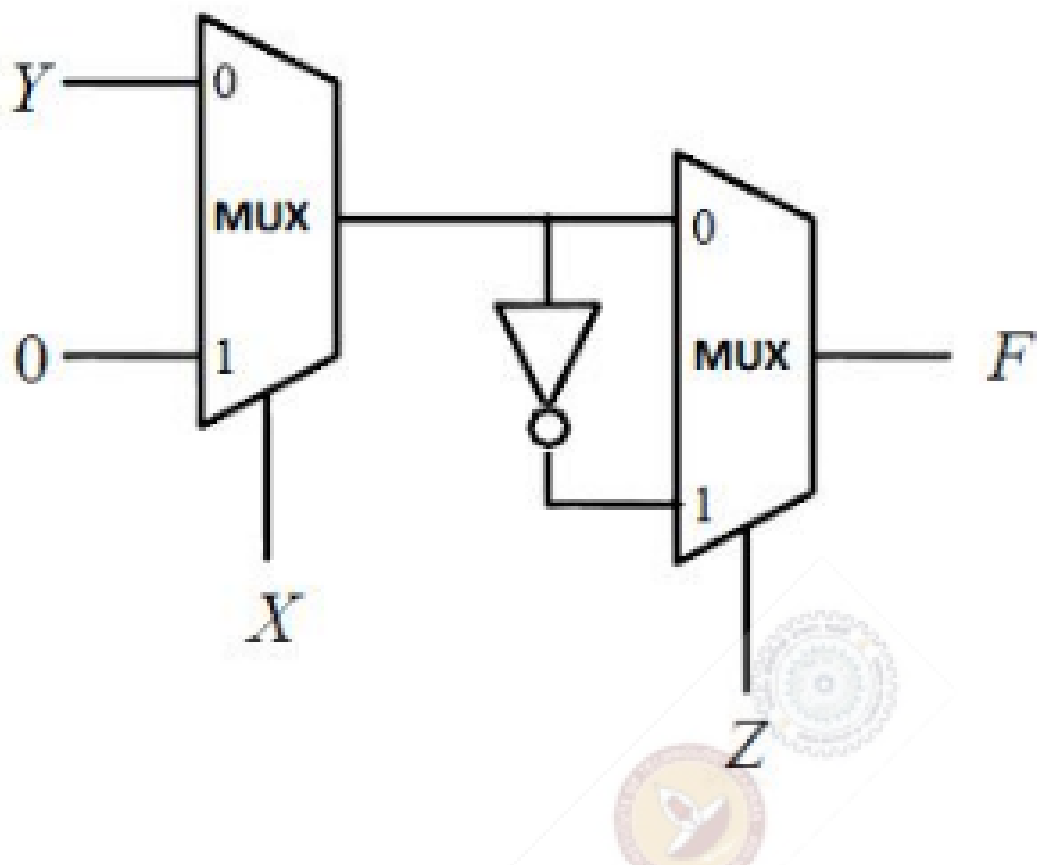


Figure 3.8:

22. Find the logic function implemented by the circuit given below in Fig. 3.9 (GATE EC 2018)

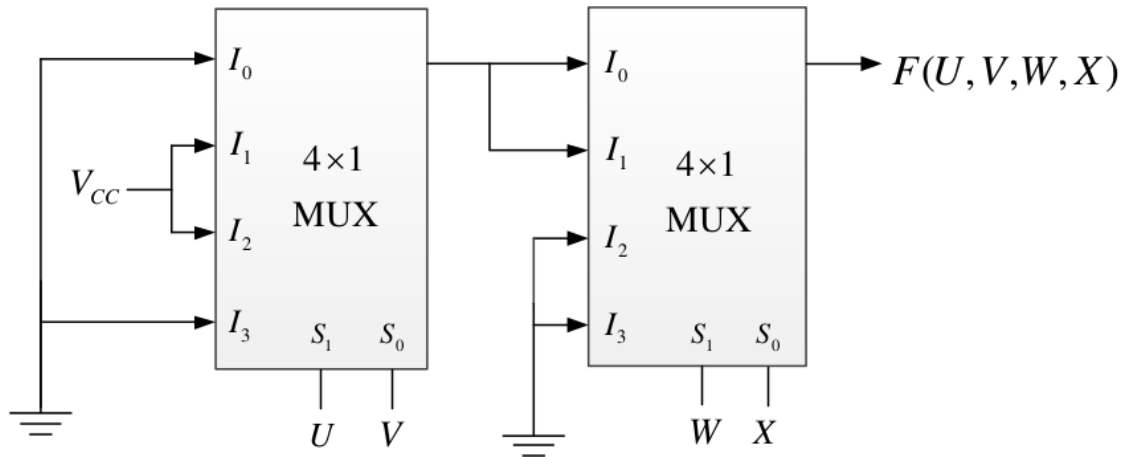


Figure 3.9:

23. Find the logic function implemented by the circuit given below in Fig. 3.10 (GATE EE 2018)

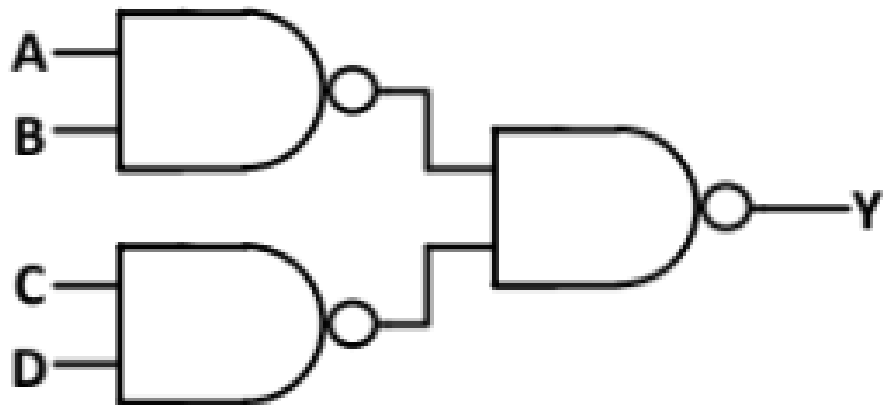


Figure 3.10:

24. Find the logic function implemented by the circuit given below in Fig. 3.11 (GATE EE 2019)

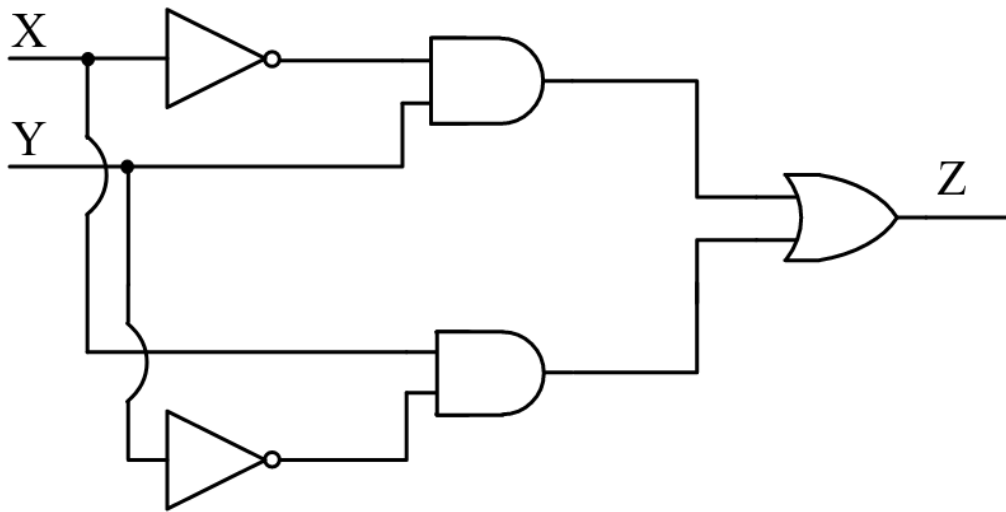


Figure 3.11:

25. Let \oplus and \odot denote the Exclusive OR and Exclusive NOR operations, respectively. Which one of the following is NOT CORRECT ? 25 (GATE CS 2018)

- (A) $\overline{P \oplus Q} = P \odot Q$
- (B) $\overline{P} \oplus Q = P \odot Q$
- (C) $\overline{P} \oplus \overline{Q} = P \oplus Q$
- (D) $(P \oplus \overline{P}) \oplus Q = (P \odot \overline{P}) \odot \overline{Q}$

26. A Boolean digital circuit is composed using two 4-input multiplexers ($M1$ and $M2$) and one 2-input multiplexer ($M3$) as shown in the figure. $X0-X7$ are the inputs of the multiplexers $M1$ and $M2$ and could be connected to either 0 or 1. The select lines of the multiplexers are connected to Boolean variables A , B and C as shown. (GATE CS2023,44)

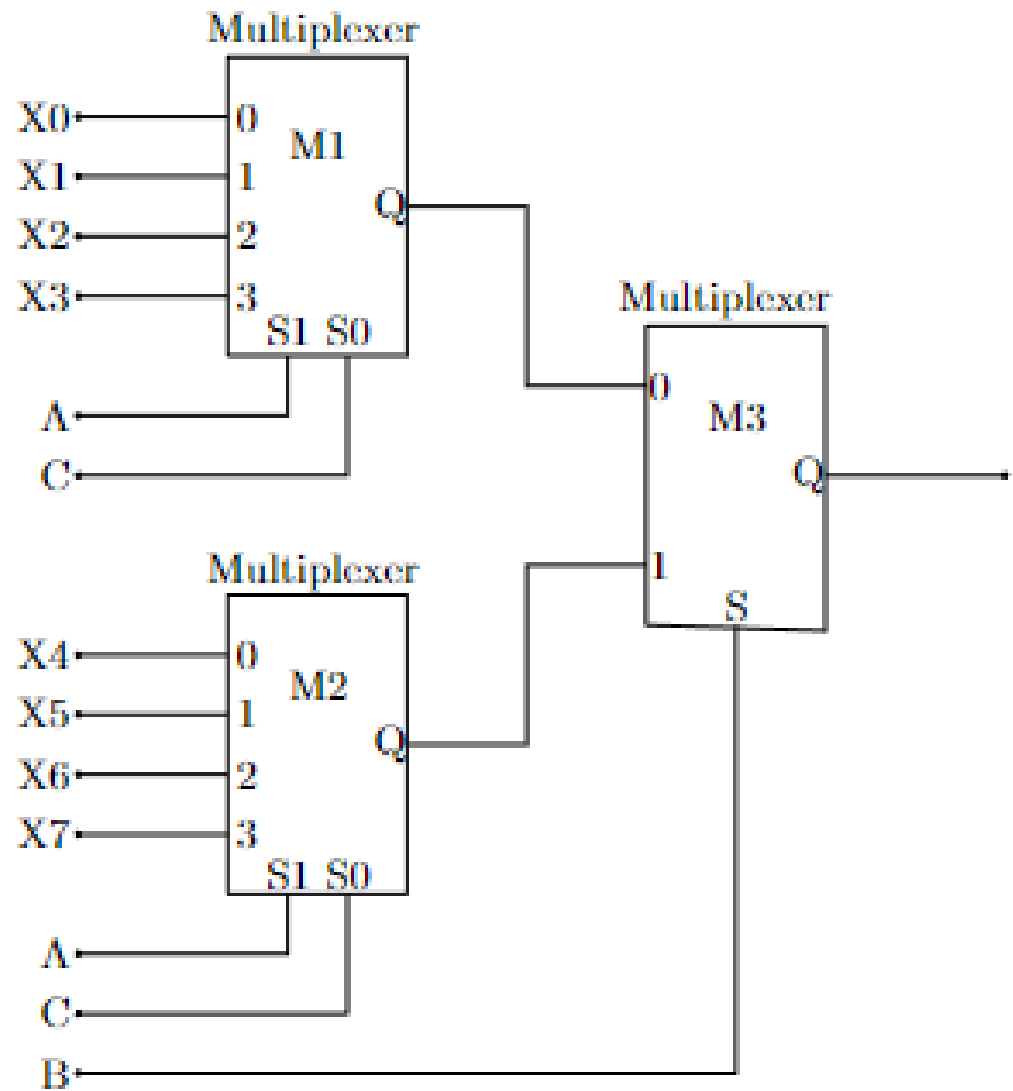


Figure 3.12: Digital Circuit

Which one of the following set of values of $(X_0, X_1, X_2, X_3, X_4, X_5, X_6, X_7)$ will realise the Boolean function $\overline{A} + \overline{A}.C + A.\overline{B}.C$?

- (a) $(1, 1, 0, 0, 1, 1, 1, 0)$

(b) (1, 1, 0, 0, 1, 1, 0, 1)

(c) (1, 1, 0, 1, 1, 1, 0, 0)

(d) (0, 0, 1, 1, 0, 1, 1, 1)

27. For the given digital circuit, $A = B = 1$. Assume that AND, OR, and NOT gates have propagation delays of 10ns, 10ns, and 5ns respectively. All lines have zero propagation delay. Given that $C = 1$ when the circuit is turned on, the frequency of steady-state oscillation of the output Y is _____. (GATE IN 2023)

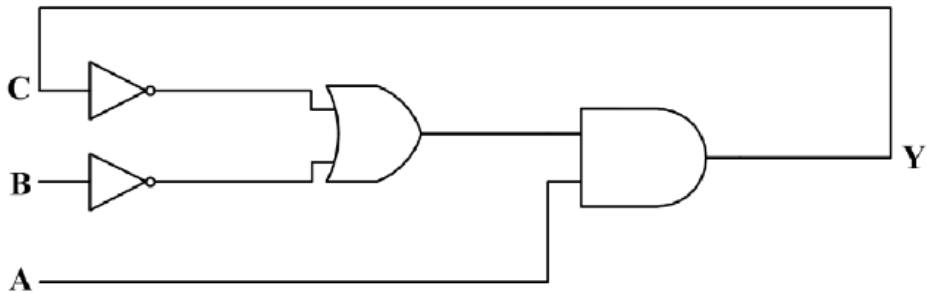


Figure 3.13: Image

(a) 20MHz

(b) 15MHz

(c) 40MHz

(d) 50MHz

28. Select the Boolean function(s) equivalent to $x + yz$, where x, y , and z are Boolean variables, and $+$ denotes logical OR operation. (GATE EC 2022)

(A) $x + z + xy$

(B) $(x + y)(x + z)$

(C) $x + xy + yz$

(D) $x + xz + xy$

29. Which one of the following options is CORRECT for the given circuit ? (GATE PHYSICS 2023)

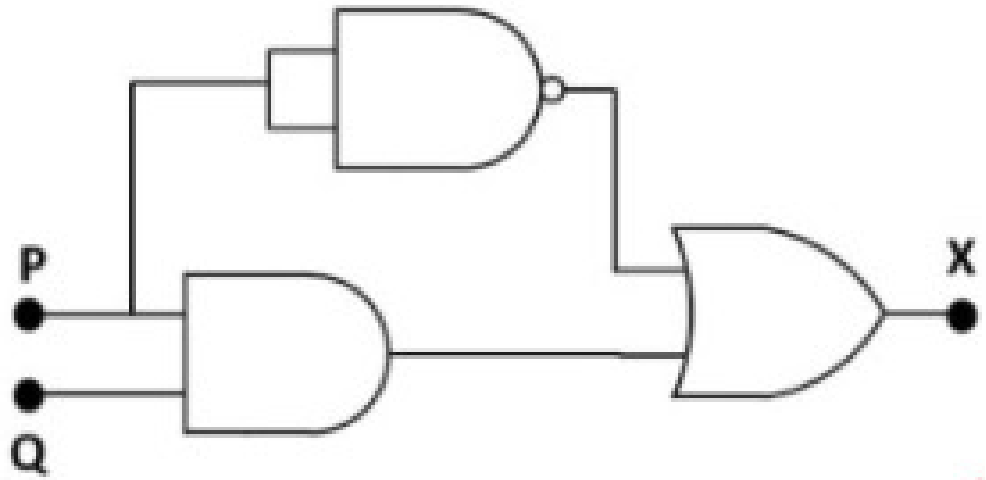


Figure 3.14:

(A) $P = 1, Q = 1 ; X = 0$

(B) $P = 1, Q = 0 ; X = 1$

(C) $P = 0, Q = 1 ; X = 0$

(D) $P = 0, Q = 0 ; X = 1$

30. In the circuit diagram shown below, the logic gates operate with a supply voltage of 1V. NAND and XNOR have 200ps and 400ps input-to-output delay, respectively.

At time $t = T$, $A(t) = 0$, $B(t) = 1$ and $Z(t) = 0$. When the inputs are changed to $A(t) = 1$, $B(t) = 0$ at $t = 2T$, a 1 V pulse is observed at Z . the pulse width of the 1V pulse is ps.

(GATE BM 2022)

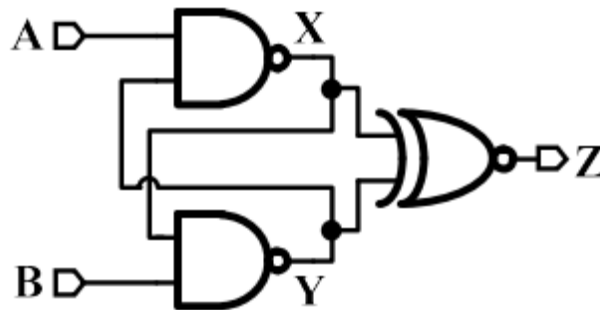


Figure 3.15:

- (a) 100
- (b) 200
- (c) 400
- (d) 600

31. Consider a Boolean gate (D) where the output (Y) is related to the inputs (A) and (B) as, $Y = A + B$, where $+$ denotes logical OR operation. The Boolean inputs '0' and '1' are also available separately. Using instances of only D gates and inputs '0' and '1', (select the correct option(s)). (GATE EC 2022)

- (a) NAND logic can be implemented
- (b) OR logic cannot be implemented
- (c) NOR logic can be implemented

(d) AND logic cannot be implemented.

32. Let $R1$ and $R2$ be two 4-bit registers that store numbers in 2's complement form. For the operation $R1 + R2$, which one of the following values of $R1$ and $R2$ gives an arithmetic overflow? (GATE CS 2022)

(a) $R1 = 1011$ and $R2 = 1110$


(b) $R1 = 1100$ and $R2 = 1010$

(c) $R1 = 0011$ and $R2 = 0100$

(d) $R1 = 1001$ and $R2 = 1111$

33. The maximum clock frequency in MHz of a 4-stage ripple counter, utilizing flip-flops, with each flip-flop having a propagation delay of 20 ns, is _____.
(round off to one decimal place) (GATE EE 2022)

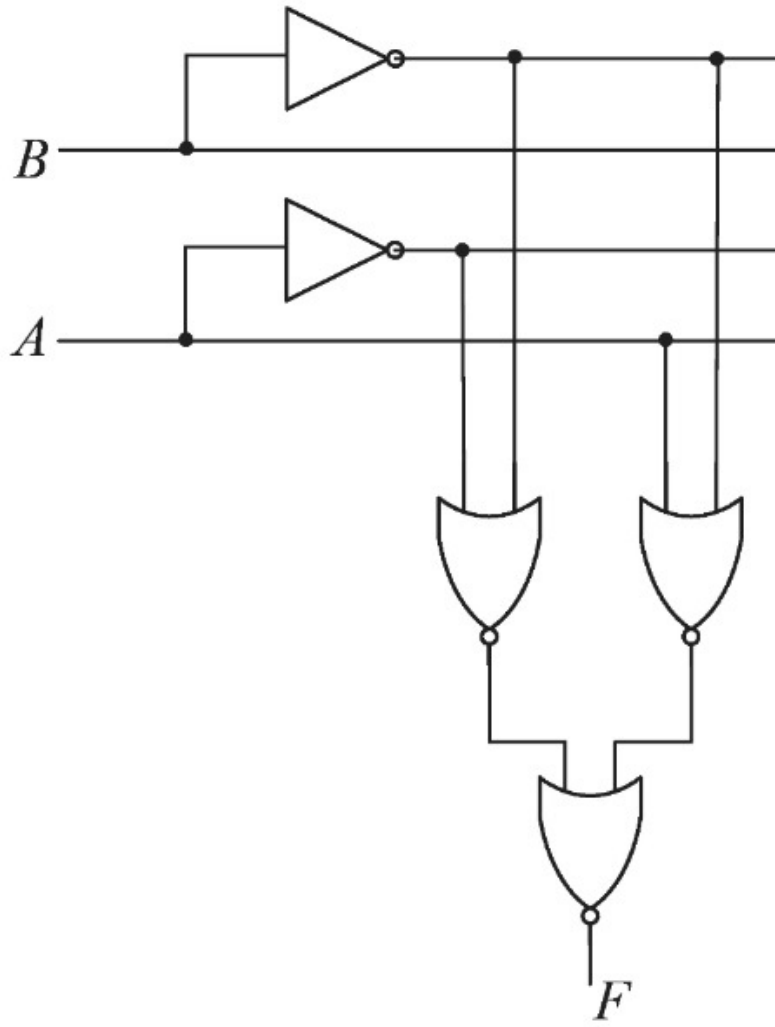34. The logic block shown has an output F given by _____. (GATE IN 2021)



(a) $A + B$

(b) $A.\bar{B}$

(c) $A + \bar{B}$

(d) \bar{B}

35. Consider the following Boolean expression

$$F = (X + Y + Z)(\bar{X} + Y)(\bar{Y} + Z)$$

Which of the following Boolean expressions is/are equivalent to \bar{F} (complement of F)?

(Gate CS 2021,42)

(a) $(\bar{X} + \bar{Y} + \bar{Z})(X + \bar{Y})(Y + \bar{Z})$

(b) $X\bar{Y} + \bar{Z}$

(c) $(X + \bar{Z})(\bar{Y} + \bar{Z})$

(d) $X\bar{Y} + Y\bar{Z} + \bar{X}\bar{Y}\bar{Z}$

36. The propagation delays of the XOR gate, AND gate and multiplexer (MUX) in the circuit shown in the figure are $4ns$, $2ns$ and $1ns$, respectively. If all the inputs P, Q, R, S and T are applied simultaneously and held constant, the maximum propagation delay of the circuit is

(GATE-EC2021,31)

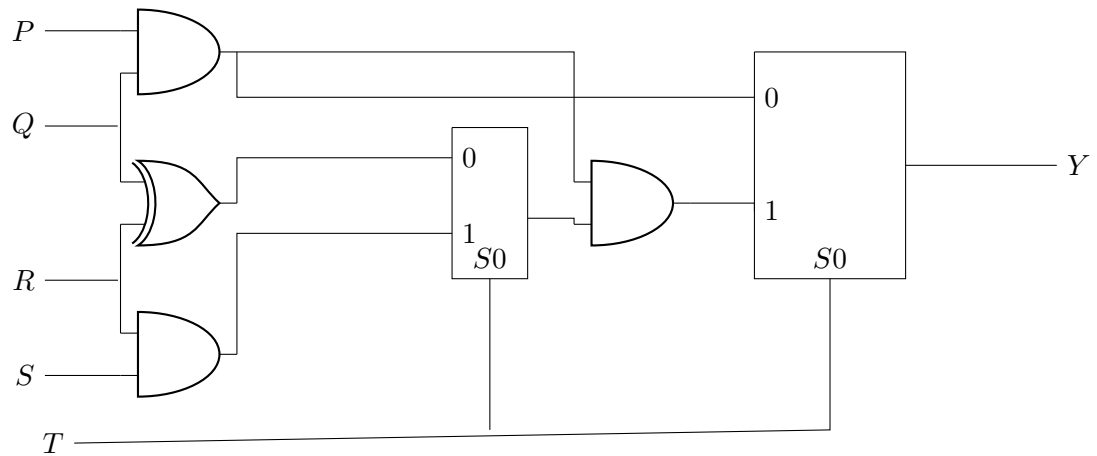


Figure 3.16: circuit daigram

(a) $3ns$

(b) $5ns$

(c) $6ns$

(d) $7ns$

37. The above combination of logic gate represent the operation (GATE PH 2021)

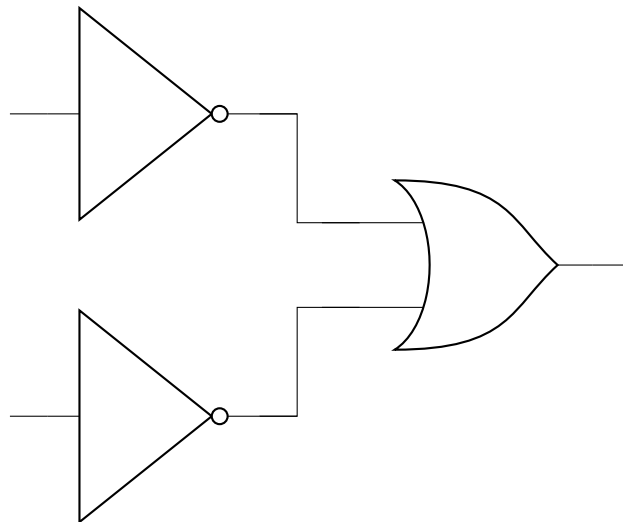


Figure 3.17: combination circuit

(a) OR

(b) NAND

(c) AND

(d) NOR

38. Consider the boolean Function $z(a, b, c)$ from below .

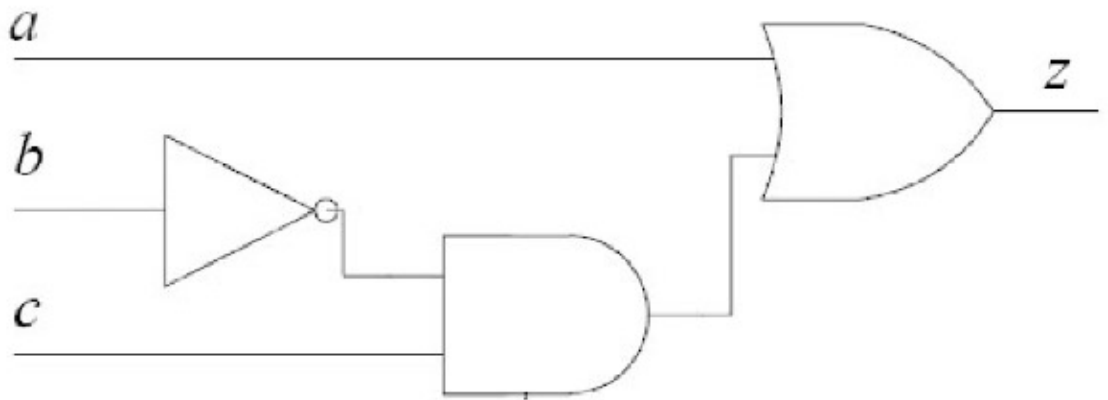



Figure 3.18: circuit diagram

(Gate CS-2020)

Which of the following minterm lists represent the circuit given above?

- (a) $z = \Sigma (0, 1, 3, 7)$
- (b) $z = \Sigma (1, 4, 5, 6, 7)$
- (c) $z = \Sigma (2, 4, 5, 6, 7)$
- (d) $z = \Sigma (2, 3, 5)$

 39. In the latch circuit shown, the NAND gates have non-zero but unequal propagation delays. The present input condition is: $P = Q = '0'$. If the input condition is changed simultaneously to $P = Q = '1'$, the outputs X and Y are



- (a) $X = '1', Y = '1'$
- (b) either $X = '1', Y = '0'$ or $X = '0', Y = '1'$
- (c) either $X = '1', Y = '1'$ or $X = '0', Y = '0'$
- (d) $X = '0', Y = '0'$

(GATE EC 2017)

40. Consider three 4-variable functions f_1, f_2 , and f_3 , which are expressed in sum-of-minterms as

$$f_1 = \sum (0, 2, 5, 8, 14), \quad f_2 = \sum (2, 3, 6, 8, 14, 15), \quad f_3 = \sum (2, 7, 11, 14)$$

For the following circuit with one AND gate and one XOR gate, the output function f can be expressed as: (GATE-CS2019,30)

 


Figure 3.19: Circuit Daigram

- (a) $\sum (7, 8, 11)$
- (b) $\sum (2, 7, 8, 11, 14)$
- (c) $\sum (2, 14)$
- (d) $\sum (0, 2, 3, 5, 6, 7, 8, 11, 14, 15)$

41. In the circuit shown, what are the values of F for $EN = 0$ and $EN = 1$, respectively?

(GATE-EC2019,14)

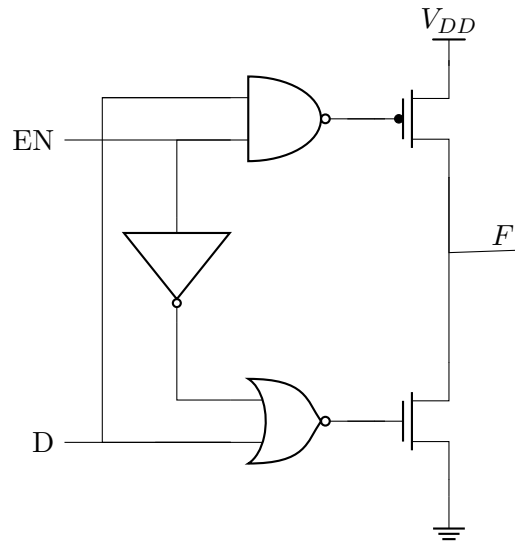


Figure 3.20: Circuit Diagram

- (a) 0 and D
- (b) $Hi - Z$ and D
- (c) 0 and 1
- (d) $Hi - Z$ and \overline{D}

42. In the circuit shown, A and B are the inputs and F is the output. What is the functionality of the circuit? (GATE-EC2019,15)

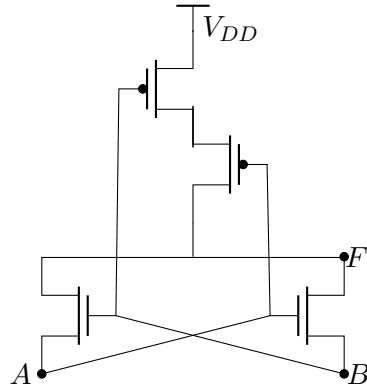


Figure 3.21: Circuit Diagram

(a) Latch

(b) XNOR

(c) SRAM Cell

(d) XOR

43. In the circuit shown below, assume that the comparators are ideal and all components have zero propagation delay. In one period of the input signal $V_{in} = 6 \sin(\omega t)$, the fraction of the time for which the output OUT is in logic HIGH is (GATE-IN2019,34)

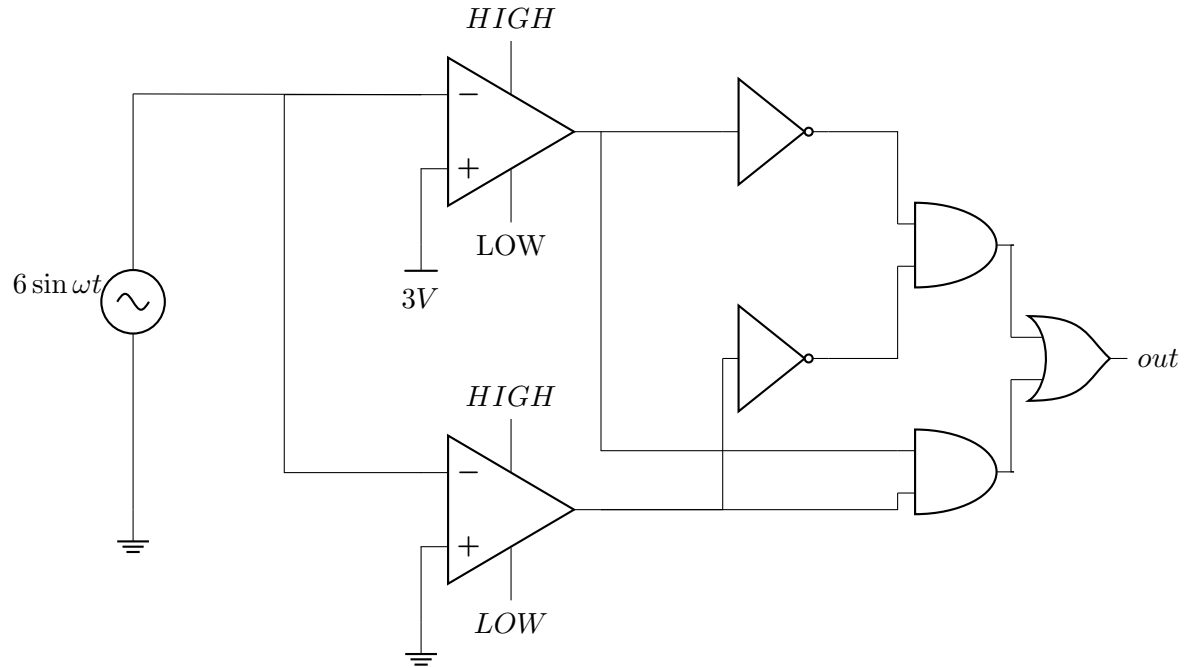


Figure 3.22: Circuit Daigram

- (a) $\frac{1}{12}$
- (b) $\frac{1}{2}$
- (c) $\frac{2}{3}$
- (d) $\frac{5}{6}$

44. The figure below shows the i th full-adder block of a binary adder circuit. C_i is the input carry and C_{i+1} is the output carry of the circuit. Assume that each logic gate has a delay of 2 nanosecond, with no additional time delay due to the interconnecting wires. If the inputs A_i , B_i ; are available and stable throughout the carry propagation, the maximum time taken for an input C_i , to produce a steady-state output C_{i+1} is ____ nanosecond. (GATE-IN2019,22)

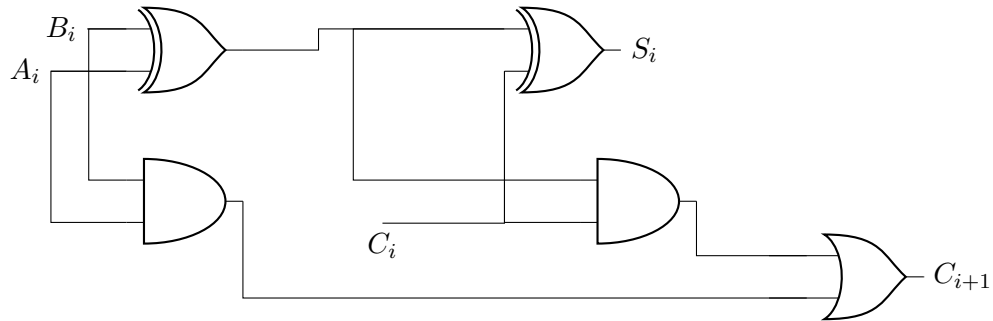


Figure 3.23: Full Adder

45. The Boolean operation performed by the following circuit at the output O is _____
 (GATE IN2020 – 12)

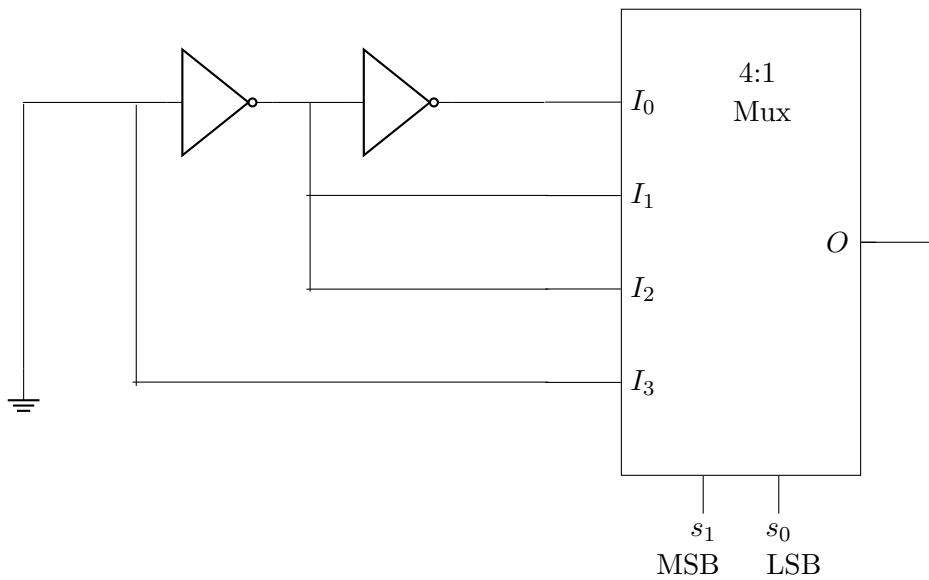


Figure 3.24: Circuit Diagram

- (a) $O = S_1 \oplus S_0$
 (b) $O = S_1 \bullet \overline{S_0}$
 (c) $O = S_1 + S_0$

(d) $O = S_0 \bullet \overline{S_1}$

46. The chip select logic for a certain DRAM chip in a memory system design is shown below. Assume that the memory system has 16 address lines denoted by A_{15} to A_0 . What is the range of addresses (in hexadecimal) of the memory system that can get enabled by the chip select (CS) signal? (GATE CS2019 – 2)

 


Figure 3.25: Logic Diagram

- (a) $C800$ to $CFFF$
- (b) $CA00$ to $CAFF$
- (c) $CA00$ to $C8FF$
- (d) $DA00$ to $DFFF$
47. A $6\frac{1}{2}$ digit time counter is set in the time period mode of operation and range is set as 'ns'. For an input signal the time-counter displays 1000000. with the same input signal, The time counter is changed to 'frequency' mode of operation and the range is set as 'HZ'. The display will show the number _____. (GATE IN2020 – 43)
48. A 2×2 ROM array is built with the help of diodes as shown in the circuit below. Here $W0$ and $W1$ are signals that select the word lines and $B0$ and $B1$ are signals that are output of the sense amps based on the stored data corresponding to the bit lines during the read operation.

 



Figure 3.26: 2×2 ROM array

(GATE EC2018,32)

During the read operation, the selected word line goes high and the other word line is in a high impedance state. As per the implementation shown in the circuit diagram above, what are the bits corresponding to D_{ij} (where $i = 0$ or 1 and $j = 0$ or 1) stored in the ROM?

- (a) $\begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$
- (b) $\begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$
- (c) $\begin{pmatrix} 1 & 0 \\ 1 & 0 \end{pmatrix}$
- (d) $\begin{pmatrix} 1 & 1 \\ 0 & 0 \end{pmatrix}$

 49. The two inputs A and B are connected to an R-S latch via two AND gates as shown in the figure. If $A = 1$ and $B = 0$, the output $Q\bar{Q}$ is



(GATE IN2017,43)

- (a) 00
 (b) 10
 (c) 01
 (d) 11
50. A and B are logical inputs and X is the logical output shown in the figure. The output X is related to A and B by

(GATE IN 2017)

 


Figure 3.27: Logic Gate Structure

A. $X = \bar{A}B + \bar{B}A$

B. $X = AB + \overline{B}A$

C. $X = AB + (\overline{B})(\overline{A})$

D. $X = (\overline{A})(\overline{B}) + \overline{B}A$

51. The functionality implemented by the circuit below is

(GATE 2016 EC)

 


Figure 3.28: Multiplexer

- A. 2-to-1 multiplexer
- B. 4-to-1 multiplexer
- C. 7-to-1 multiplexer
- D. 6-to-1 multiplexer

Chapter 4

Karnaugh Map

4.1. Introduction

We explain Karnaugh maps (K-map) by finding the logic functions for the incrementing decoder

4.2. Incrementing Decoder

The incrementing decoder takes the numbers 0, ..., 9 in binary as inputs and generates the consecutive number as output. The corresponding truth table is available in Table 3.5

4.3. Karnaugh Map

Using Boolean logic, output A in Table 3.5 can be expressed in terms of the inputs W, X, Y, Z as

$$A = W'X'Y'Z' + W'XY'Z' + W'X'YZ' + W'XYZ' + W'X'YZ + W'XYZ \quad (4.1)$$

1. K-Map for A : The expression in (4.1) can be minimized using the K-map in Fig 4.1
In Fig 4.1, the implicants in boxes 0,2,4,6 result in $W'Z'$ The implicants in boxes 0,8 result in $W'X'Y'$ Thus, after minimization using Fig 4.2, (4.1) can be expressed as

$$A = W'Z' + W'X'Y' \quad (4.2)$$

Using the fact that

$$\begin{aligned} X + X' &= 1 \\ XX' &= 0, \end{aligned} \quad (4.3)$$

derive (4.2) from (4.1) algebraically

2. K-Map for B : From Table 3.5, using boolean logic,

$$B = WX'Y'Z' + W'XY'Z' + WX'YZ' + W'XYZ' \quad (4.4)$$

Show that (4.4) can be reduced to

$$B = WX'Z' + W'XZ' \quad (4.5)$$

using Fig 4.2

3. Derive (4.5) from (4.4) algebraically using (4.3)
4. K-Map for C : From Table 3.5, using boolean logic,

$$C = WXY'Z' + W'X'YZ' + WX'YZ' + W'XYZ' \quad (4.6)$$

Show that (4.6) can be reduced to

 


Figure 4.1: K-map for A

$$C = WXY'Z' + X'YZ' + W'YZ' \quad (4.7)$$

using Fig 4.3

5. Derive (4.7) from (4.6) algebraically using (4.3)

		XW			
		00	01	11	10
ZY	00	0	1	0	1
	01	0	1	0	1
	11	0	0	0	0
	10	0	0	0	0

Figure 4.2: K-map for B

6. K-Map for D : From Table 3.5, using boolean logic,

$$D = WXYZ' + W'X'Y'Z \quad (4.8)$$

7. Minimize (4.8) using Fig 4.4

		XW			
		00	01	11	10
ZY	00	0	0	1	0
	01	1	1	0	1
	11	0	0	0	0
	10	0	0	0	0

Figure 4.3: K-map for C

8. Execute the code in

```
ide/7447/codes/inc_dec/inc_dec.cpp
```

and modify it using the K-Map equations for A,B,C and D Execute and verify

9. Display Decoder: Table 4.1 is the truth table for the display decoder in Fig. 3.1. Use K-maps to obtain the minimized expressions for a, b, c, d, e, f, g in terms of A, B, C, D

		XW			
		00	01	11	10
ZY	00	0	0	0	0
	01	0	0	1	0
	11	0	0	0	0
	10	1	0	0	0

Figure 4.4: K-map for D

with and without don't care conditions

4.4. Dont Care

We explain Karnaugh maps (K-map) using don't care conditions

D	C	B	A	a	b	c	d	e	f	g	Decimal
0	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	1	0	0	1	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0	2
0	0	1	1	0	0	0	0	1	1	0	3
0	1	0	0	1	0	0	1	1	0	0	4
0	1	0	1	0	1	0	0	1	0	0	5
0	1	1	0	0	1	0	0	0	0	0	6
0	1	1	1	0	0	0	1	1	1	1	7
1	0	0	0	0	0	0	0	0	0	0	8
1	0	0	1	0	0	0	1	1	0	0	9

Table 4.1: Truth table for display decoder.

4.5. Don't Care Conditions

1. Don't Care Conditions: 4 binary digits are used in the incrementing decoder in Table 4.1 However, only the numbers from 0-9 are used as input/output in the decoder and we don't care about the numbers from 0-5 This phenomenon can be addressed by revising the truth table in Table 4.1 to obtain Table 4.2
2. The revised K-map for A is available in Fig 4.5. Show that

$$A = W' \quad (4.9)$$

3. The revised K-map for B is available in Fig 4.6 Show that

$$B = WX'Z' + W'X \quad (4.10)$$

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	-	-	-	-
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

Table 4.2:

4. The revised K-map for C is available in Fig 4.7 Show that

$$C = X'Y + W'Y + WXY' \quad (4.11)$$

5. The revised K-map for D is available in Fig 4.8 Show that

$$D = W'Z + WXY \quad (4.12)$$

6. Verify the incrementing decoder with don't care conditions using the arduino

		XW			
		00	01	11	10
ZY	00	1	0	0	1
	01	1	0	0	1
	11	-	-	-	-
	10	1	0	-	-

Figure 4.5: K-map for A with don't cares

7. Display Decoder: Use K-maps to obtain the minimized expressions for a, b, c, d, e, f, g in terms of A, B, C, D with don't care conditions

8. Verify the display decoder with don't care conditions using arduino

		XW			
		00	01	11	10
ZY	00	0	1	0	1
	01	0	1	0	1
	11	-	-	-	-
	10	0	0	-	-

Figure 4.6: K-map for B with don't cares

4.6. Problems

1. Obtain the Minimal Form for the Boolean Expression (CBSE 2013)

$$H(P, Q, R, S) = \sum(0, 1, 2, 3, 5, 7, 8, 9, 10, 14, 15) \quad (4.13)$$

2. Write the POS form for the function G shown in Table 4.3. (CBSE 2013)

 


Figure 4.7: K-map for C with don't cares

3. Reduce the following Boolean Expression to its simplest form using K-Map (CBSE 2015)

$$F(X, Y, Z, W) = (0, 1, 4, 5, 6, 7, 8, 9, 11, 15) \quad (4.14)$$

4. Derive a Canonical POS expression for a Boolean function F , represented by the

		XW			
		00	01	11	10
ZY	00	0	0	0	0
	01	0	0	1	0
	11	-	-	-	-
	10	1	0	-	-

Figure 4.8: K-map for D with don't cares

following truth table

(CBSE 2015)

5. (CBSE 2015) Reduce the following Boolean Expression to its simplest form using K-map

$$F(X, Y, Z, W) = \sum(0, 1, 6, 8, 9, 10, 11, 12, 15) \quad (4.15)$$

U	V	W	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 4.3:

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 4.4:

6. Reduce the following Boolean Expression to its simplest form using K-map. (CBSE 2016)

$$F(X, Y, Z, W) = \sum(2, 6, 7, 8, 9, 10, 11, 13, 14, 15) \quad (4.16)$$

7. Derive a Canonical POS expression for a Boolean function F, represented in Table 4.5 (CBSE 2016)

P	Q	R	F(P, Q, R)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Table 4.5:

8. Verify the following (CBSE 2016)

$$A' + B'C = A'B'C' + A'BC' + A'BC + A'B'C + AB'C \quad (4.17)$$

9. Reduce the following boolean expression to it's simplest form using K-Map (CBSE 2017)

$$F(X, Y, Z, W) = \sum(0, 1, 2, 3, 4, 5, 10, 11, 14) \quad (4.18)$$

10. Reduce the following Boolean Expression to its simplest form using K-Map. (CBSE 2017)

$$E(U, V, Z, W) = (2, 3, 6, 8, 9, 10, 11, 12, 13) \quad (4.19)$$

11. Derive a canonical POS expression for a Boolean function G , represented by Table 4.6 (CBSE 2017)

12. Derive a canonical POS expression for a Boolean function FN , represented by Table

X	Y	Z	G(X,Y,Z)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Table 4.6:

4.7.

(CBSE 2018)

X	Y	Z	FN(X,Y,Z)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 4.7:

13. Reduce the following Boolean expression in the simplest form using K-Map.

$$F(P, Q, R, S) = \sum(0, 1, 2, 3, 5, 6, 7, 10, 14, 15) \quad (4.20)$$

(CBSE 2019)

14. Fig. 4.9 below shows a multiplexer where S0 and S1 are the select lines, I0 to I3 are the input lines, EN is the enable line and F(P,Q,R) is the output. Find the boolean

expression for output F as function of inputs P, Q, R using K-map. (GATE EC 2020)

 


Figure 4.9:

15. The four variable function f is given in terms of min-terms as

$$f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15) \quad (4.21)$$

Using the K-map minimize the function in the sum of products form. (GATE EC 1991)

16. Find the logic realized by the circuit in Fig. 4.10.

(GATE EC 1992)

 


Figure 4.10:

17. A combinational circuit has three inputs A, B and C and an output F. F is true only for the following input combinations.

(GATE EC 1992)

- (a) A is false and B is true
- (b) A is false and C is true
- (c) A, B and C are all false
- (d) A, B and C are all true

(a) Write the truth table for F. use the convention, true = 1 and false = 0.

(b) Write the simplified expression for F as a Sum of Products.

(c) Write the simplified expression for F as a product of Sums.

18. Draw the logic circuit for Table 4.8 using only NOR gates. (GATE EC 1993)

C	B	A	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Table 4.8:

19. Implement the following Boolean function in a 8x1 multiplexer. (GATE EC 1993)

$$Q = BC + ABD' + A'C'D \quad (4.22)$$

20. Minimize the following Boolean function in 4.23.

$$F = A'B'C' + A'BC' + A'BC + ABC' \quad (4.23)$$

21. Find the Boolean expression for Table 4.9. (GATE EC 2005)

22. Minimize the logic function represented by the following Karnaugh map. (CBSE

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Table 4.9:

		YZ			
		00	01	11	10
X	0	1	1	1	0
	1	0	0	1	0

2021)

23. Find the output for the Karnaugh map shown below

(GATE EE 2019)

		PQ			
		00	01	11	10
RS	00	0	1	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

24. The propagation delays of the XOR gate, AND gate and multiplexer (MUX) in the

circuit shown in the Fig. 4.11 are 4 ns, 2 ns and 1 ns, respectively. If all the inputs P, Q, R, S and T are applied simultaneously and held constant, the maximum propagation delay of the circuit is (Gate EC-2021)

- (a) 3 ns
- (b) 5 ns
- (c) 6 ns
- (d) 7 ns

 


Figure 4.11:

25. Consider the 2-bit multiplexer(MUX) shown in the figure. For output to be the XOR of R and S, the values for W, X, Y and Z are ? (GATE EC-2022)

- (a) $W = 0, X = 0, Y = 1, Z = 1$
- (b) $W = 1, X = 0, Y = 1, Z = 0$

 


Figure 4.12:

(c) $W = 0, X = 1, Y = 1, Z = 0$

(d) $W = 1, X = 1, Y = 0, Z = 0$

26. $A = a_1a_0$ and $B = b_1b_0$ are two 2-bit unsigned binary numbers. If $F(a_1, a_0, b_1, b_0)$ is a Boolean function such that $F = 1$ only when $A > B$, and $F = 0$ otherwise, then F can be minimized to the form _____. (GATE IN-2022)

27. The logic block shown has an output F given by _____. (GATE IN 2022)

 


Figure 4.13: Circuit

(a) $A + B$

(b) $A.\bar{B}$

(c) $A + \bar{B}$

(d) \bar{B}

28. A 4×1 multiplexer with two selector lines is used to realize a Boolean function F having four Boolean variables X, Y, Z , and W as shown below. S_0 and S_1 denote the least significant bit (LSB) and most significant bit (MSB) of the selector lines of the multiplexer, respectively. I_0, I_1, I_2, I_3 are the input lines of the multiplexer.

 


Figure 4.14: 4×1 multiplexer

(GATE IN-2021)

The canonical sum of product representation of F is:

(A) $F(X, Y, Z, W) = \Sigma m(0, 1, 3, 14, 15)$

(B) $F(X, Y, Z, W) = \Sigma m(0, 1, 3, 11, 14)$

(C) $F(X, Y, Z, W) = \Sigma m(2, 5, 9, 11, 14)$

(D) $F(X, Y, Z, W) = \Sigma m(1, 3, 7, 9, 15)$

29. The output expression for the Karnaugh map shown below is

(GATE EE 2019)

		PQ			
		00	01	11	10
RS	00	0	1	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

Figure 4.15:

(a) $QR' + S$

(b) $QR + S$

(c) $QR' + S'$

(d) $QR + S'$

30. In the circuit shown below , X and Y are digital inputs, and Z is a digital output. The equivalent circuit is a (GATE EE 2019)

 


Figure 4.16:

(a) NAND gate

- (b) NOR gate
- (c) XOR gate
- (d) XNOR gate

31. The output F of the digital circuit shown can be written in the form(s)_____

(GATE IN 2022)

 


Figure 4.17:

- (a) $\overline{A \cdot B}$
- (b) $\overline{A+B}$
- (c) $\overline{A + B}$
- (d) $\overline{A \cdot B}$

32. If $X = X_1X_0$ and $Y = Y_1Y_0$ are 2-bit binary numbers. The Boolean function S that satisfies the condition "If $X > Y$, then $S = 1$ ", in its minimized form, is ?

- (a) $X_1Y_1 + X_0Y_0$
- (b) $X_1\overline{Y_1} + X_0\overline{Y_0}Y_1 + X_0\overline{Y_0}X_1$
- (c) $X_1\overline{Y_1}X_0\overline{Y_0}$
- (d) $X_1Y_1 + X_0\overline{Y_0}Y_1 + X_0\overline{Y_0}X_1$

(GATE IN 2019)

33. The figure below shows the i^{th} full-adder block of a binary adder circuit. C_i is the input carry and C_{i+1} is the output carry of the circuit. Assume that each logic gate has a delay of 2 nanosecond, with no additional time delay due to the interconnecting wires. Of the inputs A_i , B_i are available and stable throughout the carry propagation, the maximum time taken for an input C_i to produce a steady-state output C_{i+1} is _____ nanosecond. (GATE IN 2019)

 


Figure 4.18:

34. The Product of sum expression of a Boolean function $F(A, B, C)$ three variables is given by

$$F(A, B, C) = (A + B + \overline{C}) \times (A + \overline{B} + \overline{C}) \times (\overline{A} + B + C) \times (\overline{A} + \overline{B} + \overline{C}) \quad (4.24)$$

The canonical sum of product expression of $F(A, B, C)$ is given by

(a) $\overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C} + ABC$

(b) $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C + ABC$

(c) $AB\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}C$

(d) $\bar{A}\bar{B}\bar{C} + \bar{A}BC + AB\bar{C} + ABC$

(GATE IN 2018)

35. A four-variable Boolean function is realized using 4×1 multiplexers as shown in the figure.

 


Figure 4.19:

The minimized expression for

(a) $(UV + \bar{U}\bar{V}) \bar{W}$

(b) $(UV + \bar{U}\bar{V}) (\bar{W}\bar{X} + \bar{W}X)$

(c) $(U\bar{V} + \bar{U}V) \bar{W}$

(d) $(U\bar{V} + \bar{U}V) (\bar{W}\bar{X} + \bar{W}X)$

(GATE EC 2018)

36. A function $F(A, B, C)$ defined by three Boolean variables A, B and C when expressed as sum of products is given by

$F = (\overline{A} \cdot \overline{B} \cdot \overline{C}) + (\overline{A} \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot \overline{C})$ where, \overline{A} , \overline{B} and \overline{C} are the complements of the respective variables. The product of sums (POS) form of the function F is

- (A) $(A + B + C) \cdot (A + \overline{B} + C) \cdot (\overline{A} + B + C)$
- (B) $(\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (A + \overline{B} + \overline{C})$
- (C) $(A + B + \overline{C}) \cdot (A + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + C) \cdot (\overline{A} + \overline{B} + C)$
- (D) $(\overline{A} + \overline{B} + C) \cdot (\overline{A} + B + C) \cdot (A + \overline{B} + C) \cdot (A + B + \overline{C}) \cdot (A + B + C)$

(GATE EC 2018)

37. In the Karnaugh map shown below, X denotes a don't care term. What is the minimal form of the function represented by the Karnaugh map?


		<i>ba</i>			
		00	01	11	10
<i>cd</i>	00	1	1	0	1
	01	X	0	0	0
	11	X	0	0	0
	10	1	1	0	X

- (A) $b'd' + a'd'$
- (B) $a'b' + b'd' + a'bd'$
- (C) $b'd' + a'bd'$
- (D) $a'b' + b'd' + a'd'$

(GATE EC 2008)

38. In the circuit shown below, assume that the comparators are ideal and all components have zero propagation delay. In one period of the input signal $V_{in} = 6\sin(\omega t)$, the fraction of the time which the output OUT is in logic state HIGH


is

 

- (a) $\frac{1}{12}$
- (b) $\frac{1}{2}$
- (c) $\frac{2}{3}$
- (d) $\frac{5}{6}$

(GATE EC 2018)

 39. The Boolean function $F(X, Y)$ realized by the given circuit is



- (a) $\bar{X}Y + X\bar{Y}$
- (b) $\bar{X}\bar{Y} + XY$

(c) $X + Y$

(d) $\bar{X}.\bar{Y}$

(GATE IN 2019)


40. Consider the minterm list form of a Boolean function given below.

$$F(P, Q, R, S) = \sum m(0, 2, 5, 7, 9, 11) + d(3, 8, 10, 12, 14)$$

Here, m denotes a minterm and d denotes a don't care term. The number of essential prime implicants of the function is

(GATE CS 2018)

 41. In the circuit shown below, P and Q are the inputs. The logical function realized by the circuit shown below



(a) $Y=PQ$

(b) $Y = P + Q$

(c) $Y = \overline{PQ}$

(d) $Y = \overline{P + Q}$

(GATE EC2023,23)

 


Figure 4.20: k-maps

Fig. 1

(a) $P = 1, Q = 1; X = 0$

(b) $P = 1, Q = 0; X = 0$

(c) $P = 0, Q = 1; X = 0$

(d) $P = 0, Q = 0; X = 1$

(GATE PH2023,24)

42. Consider the 2-bit multiplexer(MUX) shown in the figure. For OUTPUT to be the XOR of C and D, the values for A_0, A_1, A_2 and A_3 are ____ (GATE EC 2022)

 


Figure 4.21: MUX

- (A) $A_0 = 0, A_1 = 0, A_2 = 1, A_3 = 1$
- (B) $A_0 = 1, A_1 = 0, A_2 = 1, A_3 = 0$
- (C) $A_0 = 0, A_1 = 1, A_2 = 1, A_3 = 0$
- (D) $A_0 = 1, A_1 = 1, A_2 = 0, A_3 = 0$

43. The simplified form of the Boolean function

$F(W, X, Y, Z) = \sum(4, 5, 10, 11, 12, 13, 14, 15)$ with the minimum number of terms
and smallest number of literals in each terms is _____

- (a) $WX + \bar{W}X\bar{Y} + W\bar{X}Y$
- (b) $WX + WY + X\bar{Y}$
- (c) $X\bar{Y} + WY$
- (d) $\bar{X}Y + \bar{W}\bar{Y}$

(GATE IN 2023)

44. Q, R, S are Boolean variables \oplus and is the XOR operator. Select the CORRECT option(s).

- (a) $(Q \oplus R) \oplus S = Q \oplus (R \oplus S)$
- (b) $(Q \oplus R) \oplus S = 0$ when any of the Boolean variables (Q, R, S) are 0 and the third variable is 1
- (c) $(Q \oplus R) \oplus S = 1$ when $Q = R = S = 1$
- (d) $((Q \oplus R) \oplus (R \oplus S)) \oplus (Q \oplus S) = 1$

(Gate BM 2023)

45. The output F of the digital circuit shown can be written in the form(s)_____

 


Figure 4.22:

- (a) $\overline{A.B}$

(b) $\bar{A} + \bar{B}$

(c) $\overline{A + B}$

(d) $\bar{A} \cdot \bar{B}$

(GATE IN 2022)

46. $\mathbf{A} = a_1a_0$ and $\mathbf{B} = b_1b_0$ are two 2-bit unsigned binary numbers. If $\mathbf{F}(a_1, a_0, b_1, b_0)$ is a Boolean function such that $\mathbf{F} = 1$ only when $\mathbf{A} > \mathbf{B}$, and $\mathbf{F} = 0$ otherwise, then \mathbf{F} can be minimized to the form _____

(a) $a_1\bar{b}_1 + a_1a_0\bar{b}_0$

(b) $a_1\bar{b}_1 + a_1a_0\bar{b}_0 + a_0\bar{b}_0\bar{b}_1$

(c) $a_1a_0\bar{b}_0 + a_0\bar{b}_0\bar{b}_1$

(d) $a_1\bar{b}_1 + a_1a_0\bar{b}_0 + a_0\bar{b}_0b_1$

(GATE IN-2022)

47. The minimum number of two-input NAND gates required to implement the following Boolean expression is _____

$$Y = [A\bar{B}(C + BD) + \bar{A}\bar{B}]C$$

(GATE-PH-2022)

48. In the circuit shown below, Y is a 2-bit (Y_1Y_0) output of the combinational logic. What is the maximum value of Y for any given digital inputs, A_1A_0 and B_1B_0 ?

(GATE-BM2021)

 


Figure 4.23:

- (A) 01
- (B) 10
- (C) 00
- (D) 11

49. Match the Boolean expression with its minimal realization. (GATE BM 2020)

	Boolean expression		Minimal realization
P	$\bar{X}\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}YZ$	K	$X(Y + Z)$
Q	$XYZ + X\bar{Y}Z + XY\bar{Z}$	L	$\bar{X}(Y + \bar{Z})$
R	$XY + XYZ + XY\bar{Z} + \bar{X}YZ$	M	Z
S	$\bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$	N	$Y(X + Z)$

- (A) $P - K, Q - L, R - N, S - M$
- (B) $P - L, Q - K, R - N, S - M$
- (C) $P - L, Q - N, R - M, S - K$
- (D) $P - M, Q - K, R - L, S - N$

50. A 4×1 multiplexer with two selector lines is used to realize a Boolean function F having four Boolean variables X, Y, Z and W as shown below. S_0 and S_1 denote the least significant bit (LSB) and most significant bit (MSB) of the selector lines of the multiplexer respectively. I_0, I_1, I_2, I_3 are the input lines of the multiplexer.

(GATE-IN2021,35)

 


Figure 4.24: Multiplexer

The canonical sum of product representations of F is

$$(a) \quad F(X, Y, Z, W) = \sum m(0, 1, 3, 14, 15)$$

(b) $F(X, Y, Z, W) = \sum m(0, 1, 3, 11, 14)$

(c) $F(X, Y, Z, W) = \sum m(2, 5, 9, 11, 14)$

(d) $F(X, Y, Z, W) = \sum m(1, 3, 7, 9, 15)$

51. The output expression for the Karnaugh map shown below is (GATE-EE2019,35)

		PQ			
		00	01	11	10
RS	00	0	1	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

Figure 4.25: K-MAP

(a) $Q\overline{R} + S$

(b) $Q\overline{R} + \overline{S}$

(c) $QR + S$

(d) $QR + \overline{S}$

52. The Boolean expression for the shaded regions as shown in the figure is _____.

(GATE IN2020 – 11)

 


Figure 4.26: Venn Diagram

(a) $(A + B) \bullet (\bar{A} + \bar{B})$

(b) $(A + \bar{B}) \bullet (\bar{A} + B)$

(c) $(\bar{A} + B) \bullet (\bar{A} + \bar{B})$

(d) $(\bar{A} + \bar{B}) \bullet (A + \bar{B})$

53. The output expression of the Karnaugh map shown below is (GATE EE-2017, 36)

AB \ CD	CD			
	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	1	1
10	0	0	0	0

s

A. $B\bar{D} + BCD$

B. $B\overline{D} + AB$

C. $\overline{B}D + ABC$

D. $B\overline{D} + ABC$

54. A Boolean function F of three variables X, Y , and Z is given as

$$F(X, Y, Z) = (X' + Y + Z) \cdot (X + Y' + Z') \cdot (X' + Y + Z') \cdot (X'Y'Z' + X'YZ' + XYZ')$$

Which one of the following is true? (GATE IN2021,31)

(a) $F(X, Y, Z) = (X + Y + Z') \cdot (X' + Y' + Z')$

(b) $F(X, Y, Z) = (X' + Y) \cdot (X + Y' + Z')$

(c) $F(X, Y, Z) = X'Z' + YZ'$

(d) $F(X, Y, Z) = X'Y'Z + XYZ$

55. The figure below shows a multiplier where S_1 and S_0 are select lines, I_0 to I_3 are the input data lines, EN is the enable line, and $F(P, Q, R)$ is the output. F is

 


Figure 4.27:

(GATE EC 2020)

(A) $PQ + \bar{Q}R.$

(B) $P + Q\bar{R}.$

(C) $P\bar{Q}R + \bar{P}Q.$

(D) $\bar{Q} + PR.$

Chapter 5

7474

We show how to use the 7474 D-Flip Flop ICs in a sequential circuit to realize a decade counter.

5.1. Components

Component	Value	Quantity
Breadboard		1
Resistor	$\geq 220\Omega$	1
Arduino	Uno	1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
Jumper Wires		20

Table 5.1:

5.2. Decade Counter

1. Generate the CLOCK signal using the **blink** program.

	INPUT				OUTPUT				CLOCK	5V			
	W	X	Y	Z	A	B	C	D					
Ar-duino	D6	D7	D8	D9	D2	D3	D4	D5	D13				
7474	5	9			2	12			CLK1CLK2	1	4	10	13
7474			5	9			2	12	CLK1CLK2	1	4	10	13
7447					7	1	2	6		16			

Table 5.2:

2. Connect the Arduino, 7447 and the two 7474 ICs according to Table 5.2 and Fig. 5.2.

The pin diagram for 7474 is available in Fig. 5.1

 


Figure 5.1:

3. Realize the decade counter in Fig. 5.2.

5.3. Problems

1. A counter is constructed with three D flip-flops. The input-output pairs are named (D_0, Q_0) , (D_1, Q_1) , and (D_2, Q_2) , where the subscript 0 denotes the least significant bit. The output sequence is desired to be the Gray-code sequence 000, 001, 011, 010, 110, 111, 101, and 100, repeating periodically. Note that the bits are listed in the $Q_2 Q_1 Q_0$ format. The combinational logic expression for D_1 is (GATE-EE2021,37)

- (a) $Q_2 Q_1 Q_0$
- (b) $Q_2 Q_0 + Q_1 \bar{Q}_0$
- (c) $\bar{Q}_2 Q_0 + Q_1 \bar{Q}_0$
- (d) $Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1$

2. The propagation delay of the exclusive-OR(XOR) gate in the circuit in the figure is 3 ns. The propagation delay of all the flip-flops is assumed to be zero. The Clock(clk) frequency provided to the circuit is 500 MHz.

 



Figure 5.3: Propagation Delay

Starting from the initial value of the flip-flop outputs $Q_2Q_1Q_0 = 111$ with $D_2 = 1$, the minimum number of triggering clock edges after which the flip-flop outputs $Q_2Q_1Q_0$ becomes 1 0 0 (in integer) is ____

(GATE-EC2021,46)

3. The maximum clock frequency in MHz of a 4-stage ripple counter, utilizing flip-flops, with each flip-flop having a propagation delay of 20 ns, is _____. (round off to one decimal place) (GATE EE 2022)


4. The digital circuit shown _____

 

- (A) is a divide-by-5 counter
 (B) is a divide-by-7 counter
 (C) is a divide-by-8 counter
 (D) does not function as a counter due to disjoint cycles of states

GATE IN 2022

 5. The propagation delay of the exclusive-OR(XOR) gate in the circuit in the figure is 3ns. The propagation delay of all the flip-flops is assumed to be zero. The clock(Clk) frequency provided to the circuit is 500MHz. (GATE EC 2021)



Starting from the initial value of the flip-flop outputs $Q_2Q_1Q_0 = 111$ with $D_2 = 1$, the minimum number of triggering clock edges after which the flip-flop outputs $Q_2Q_1Q_0$ becomes 100 (*in integer*) is ____

6. For the 3-bit binary counter shown in the figure, the output increments at every positive transition in the clock (CLK). Assume ideal diodes and the starting state of the counter as 000. If output high is $1V$ and output low is $0V$, the current I (in mA) flowing through the 50Ω resistor during the 5th clock cycle is (up to one decimal place) (GATE IN 2018)

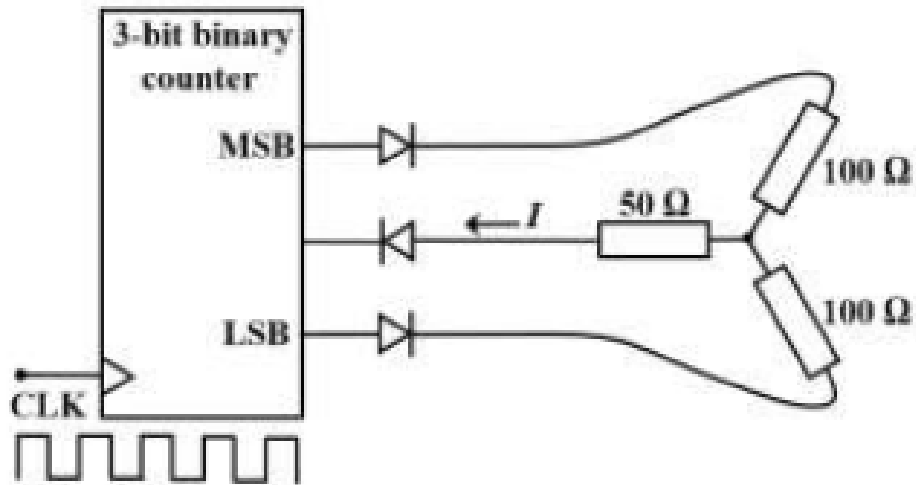


Figure 5.4: circuit

7. Consider the sequential circuit shown in the figure, where both flip-flops used are positive edge-triggered D flip-flops.


 


Figure 5.5: ckt

 
8. The number of states in the state transition diagram of this circuit that have a transition back to the same state on some value of "in" is _____. (GATE IN 2018)
9. The synchronous sequential circuit shown below works at a clock frequency of 1GHz . The throughput, in Mbits/s , and the latency, in ns , respectively, are



- (a) 1000, 3
- (b) 333.33, 1
- (c) 2000, 3
- (d) 333.33, 3

(GATE EC 2023)

 10. In a given sequential circuit, initial states are $Q_1 = 1$ and $Q_2 = 0$. For a clock frequency of 1MHz , the frequency of signal Q_2 in kHz, is (rounded off to the nearest integer)



(GATE EC 2023)

11. Neglecting the delays due to the logic gates in the circuit shown in figure, the decimal equivalent of the binary sequence $[ABCD]$ of initial logic states, which will not change with clock, is _____.

(EE GATE 2023)

 


Figure 5.6: Neglecting the delays

12. Consider a sequential digital circuit consisting of T flip-flops and D flip-flops as shown in the figure. CLKIN is is the clock input to the circuit. At the beginning, Q1, Q2 and Q3 have values 0, 1 and 1, respectively. (GATE CS2023, 43)

 


Figure 5.7: Flip-Flop

Which of the given values of (Q_1, Q_2, Q_3) can NEVER be obtained with this digital circuit?

- (a) $(0, 0, 1)$
- (b) $(1, 0, 0)$
- (c) $(1, 0, 1)$
- (d) $(1, 1, 1)$

13. In the circuit shift, the initial binary content of the shift register A 1101 and that of shift register B is 1010 The shift registers are positive edge triggered, and the gates have no delay. when the shift control is high, what will be the binary content of the shift registers A and B after clock pulses?

(GATE IN 2023)

 


Figure 5.8: circuit Digram

- (a) $A = 1101, B = 1101$
 - (b) $A = 1110, B = 1001$
 - (c) $A = 0101, B = 1101$
 - (d) $A = 1010, B = 1111$
14. For the circuit shown, the clock frequency is f_0 and the duty cycle is 25%. For the signal at the Q output of the Flip-Flop, _____. (GATE EC 2022)
- (a) frequency is $\frac{f_0}{4}$ and duty cycle is 50%
 - (b) frequency is $\frac{f_0}{4}$ and duty cycle is 25%
 - (c) frequency is $\frac{f_0}{2}$ and duty cycle is 50%
 - (d) frequency is f_0 and duty cycle is 25%
15. In the circuit shown, the initial binary content of shift register A is 1101 and that of shift register B is 1010. The shift registers are positive edge triggered, and the gates have no delay.

When the shift control is high, what will be the binary content of the shift registers A and B after four clock pulses? (Gate IN 2023)

 


Figure 5.10: Shift register

(a) A=1101,B=1101

(b) A=1110,B=1001

(c) A=0101,B=1101

(d) A=1010,B=1111

 


Figure 5.11:

- (a) is a divide-by-5 counter
- (b) is a divide-by-7 counter
- (c) is a divide-by-8 counter
- (d) does not function as a counter due to disjoint cycles of states

(GATE-IN-2022)

17. Given below is the diagram of a synchronous sequential circuit with one $J - K$ flip-flop and one T flip-flop with their outputs denoted as A and B respectively, with $J_A = (A' + B')$, $K_A = (A + B)$ and $T_B = A$. Starting from the initial state ($AB = 00$), the sequence of states (AB) visited by the circuit is

(GATE-IN-2021)

 


Figure 5.12: synchronous

- (a) $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \dots$
- (b) $00 \rightarrow 10 \rightarrow 01 \rightarrow 11 \rightarrow 00 \dots$
- (c) $00 \rightarrow 10 \rightarrow 11 \rightarrow 01 \rightarrow 00 \dots$
- (d) $00 \rightarrow 01 \rightarrow 11 \rightarrow 00 \dots$

18. Consider the *D*-Latch shown in the figure, which is transparent when its clock input *CK* is high and has zero propagation delay. In the figure, the clock signal *CLK1* has 50% duty cycle and *CLK2* is a one fifth period delayed version of *CLK1*. The duty cycle at the output of the latch in percentage is. (GATE-EC2017)

19. A 4-bit shift register circuit configured for right-shift operation, i.e.

$D_{in} \rightarrow A, A \rightarrow B, B \rightarrow C, C \rightarrow D$, is shown. If the present state of the shift register is $ABCD = 1101$, the number of clock cycles required to reach the state $ABCD = 1111$ is

(GATE-EC 2017)

 


Figure 5.14:

20. In the circuit shown, the clock frequency, i.e., the frequency of the clk signal, is 12 KHz. The frequency of the signal at **Q2** is ____ KHz. (GATE-EC2019,25)


 


Figure 5.15: Circuit Daigram

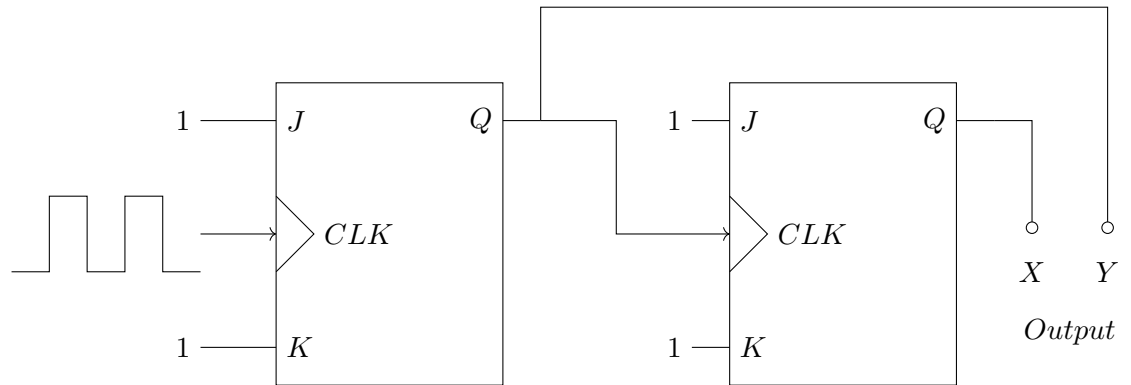21. The circuit shown in the figure below uses ideal positive edge-triggered synchronous $J - K$ flip flops with outputs X and Y . If the initial state of the output is $X = 0$ and $Y = 0$ just before the arrival of the first clock pulse, the state of the output just before the arrival of the second clock pulse is (GATE-IN2019,12)



(a) $X = 0, Y = 0$

(b) $X = 0, Y = 1$

(c) $X = 1, Y = 0$

(d) $X = 1, Y = 1$

22. Consider a 4-bit counter constructed out of four flip-flops. It is formed by connecting the J and K inputs to logic high and feeding the Q output to the clock input of the following flip-flop (see the figure). The input signal to the counter is a series of square pulses and the change of state is triggered by the falling edge. At time $t=t_0$ the outputs are in logic low state ($Q_0 = Q_1 = Q_2 = Q_3 = 0$). Then at $t=t_1$, the logic state of the outputs is

(GATE-PH2020,30)

 
 


Figure 5.16: Ripple Counter

- (a) $Q0 = 1, Q1 = 0, Q2 = 0$ and $Q3 = 0$
- (b) $Q0 = 0, Q1 = 0, Q2 = 0$ and $Q3 = 1$
- (c) $Q0 = 1, Q1 = 0, Q2 = 1$ and $Q3 = 0$
- (d) $Q0 = 0, Q1 = 1, Q2 = 1$ and $Q3 = 1$

23. Two T-flip flops are interconnected as shown in the figure. The present state of the

flip flops are: $A = 1$, $B = 1$. The input x is given as 1, 0, 1 in the next three clock cycles. The decimal equivalent of $(ABx)_2$ with A being the MSB and x being the LSB, after the 3rd clock cycle is _____. (GATE IN2020 – 40)

 


Figure 5.17: Circuit Diagram

24. For the components in the sequential circuit shown below, t_{pd} is the propagation delay, t_{setup} is the setup time, and t_{hold} is the hold time. The maximum clock frequency (rounded off to the nearest integer) at which the given circuit can operate reliably is _____ MHz. (GATE EC2020 – 50)

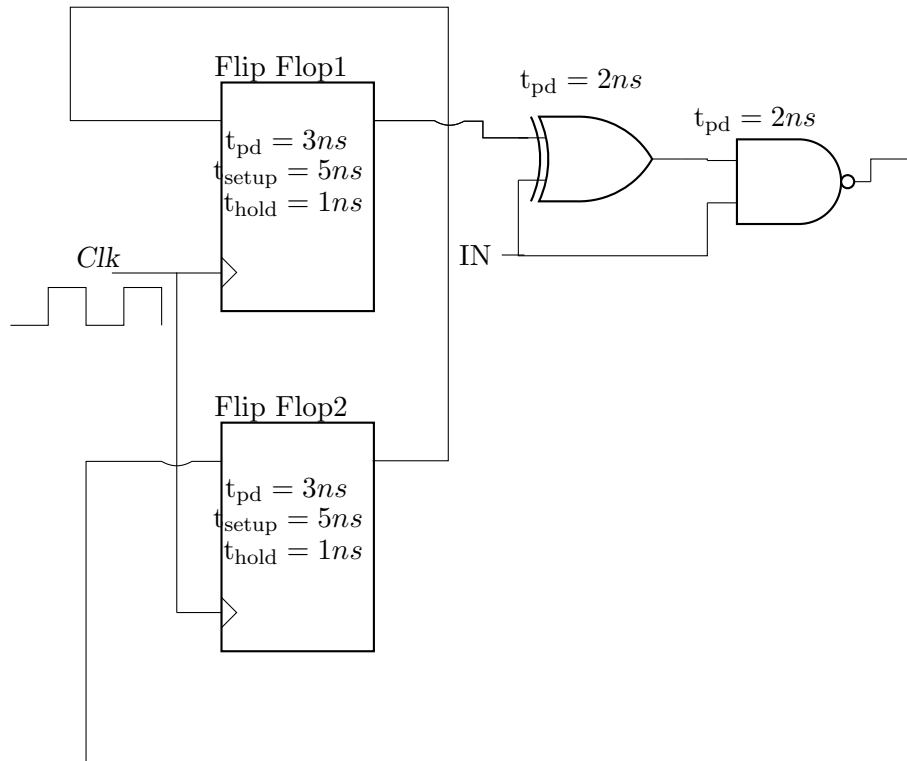


Figure 5.18: Circuit Diagram

25. A 2-bit synchronous counter using two J-K flip flops is shown. The expression for the inputs to the J-K flip flops are also shown in the figure. The output sequence of the counter starting from $Q_1Q_2 = 00$ is

GATE-IN2018,44

- A. $00 \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00 \dots$
- B. $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \dots$
- C. $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \dots$
- D. $00 \rightarrow 10 \rightarrow 11 \rightarrow 01 \rightarrow 00 \dots$

 


Figure 5.2:

 


Figure 5.9: Circuit


 


Figure 5.13:

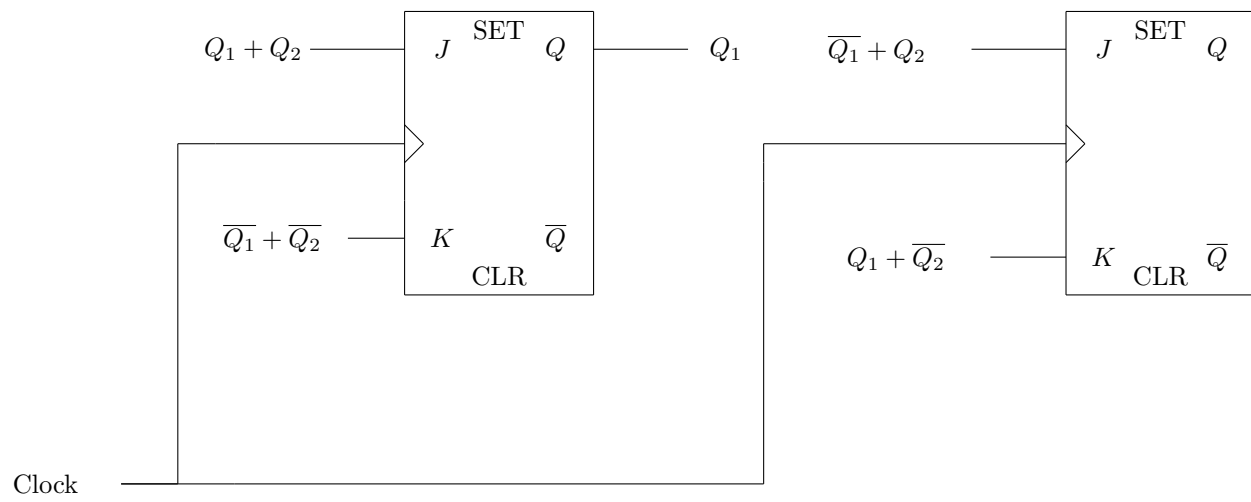

Chapter 6

Finite State Machine

We explain a state machine by deconstructing the decade counter

6.1. The Decade Counter

The block diagram of a decade counter (repeatedly counts up from 0 to 9) is available in Fig 5.2 The incrementing decoder and display decoder are part of combinational logic, while the delay is part of sequential logic

6.2. Finite State Machine

1. Fig 6.1 shows a finite state machine (FSM) diagram for the decade counter in Fig 5.2 s_0 is the state when the input to the incrementing decoder is 0 The state transition table for the FSM is Table 3.5, where the present state is denoted by the variables W, X, Y, Z and the next state by A, B, C, D .
2. The FSM implementation is available in Fig 6.2 The flip-flops hold the input for the time that is given by the clock This is nothing but the implementation of the Delay block in Fig 5.2

 


Figure 6.1: FSM for the decade counter

3. The hardware cost of the system is given by

$$\text{No of D Flip-Flops} = \lceil \log_2 (\text{No of States}) \rceil \quad (6.1)$$

For the FSM in Fig 6.1, the number of states is 10, hence the number flipflops required
 $= 4$

4. Draw the state transition diagram for a decade down counter (counts from 9 to 0 repeatedly) using an FSM
5. Write the state transition table for the down counter
6. Obtain the state transition equations with and without don't cares
7. Verify your design using an arduino

6.3. Problems

1. The digital circuit shown in Fig. 6.3 generates a modified clockpulse at the output.
 Sketch the output waveform. (GATE EE 2004)

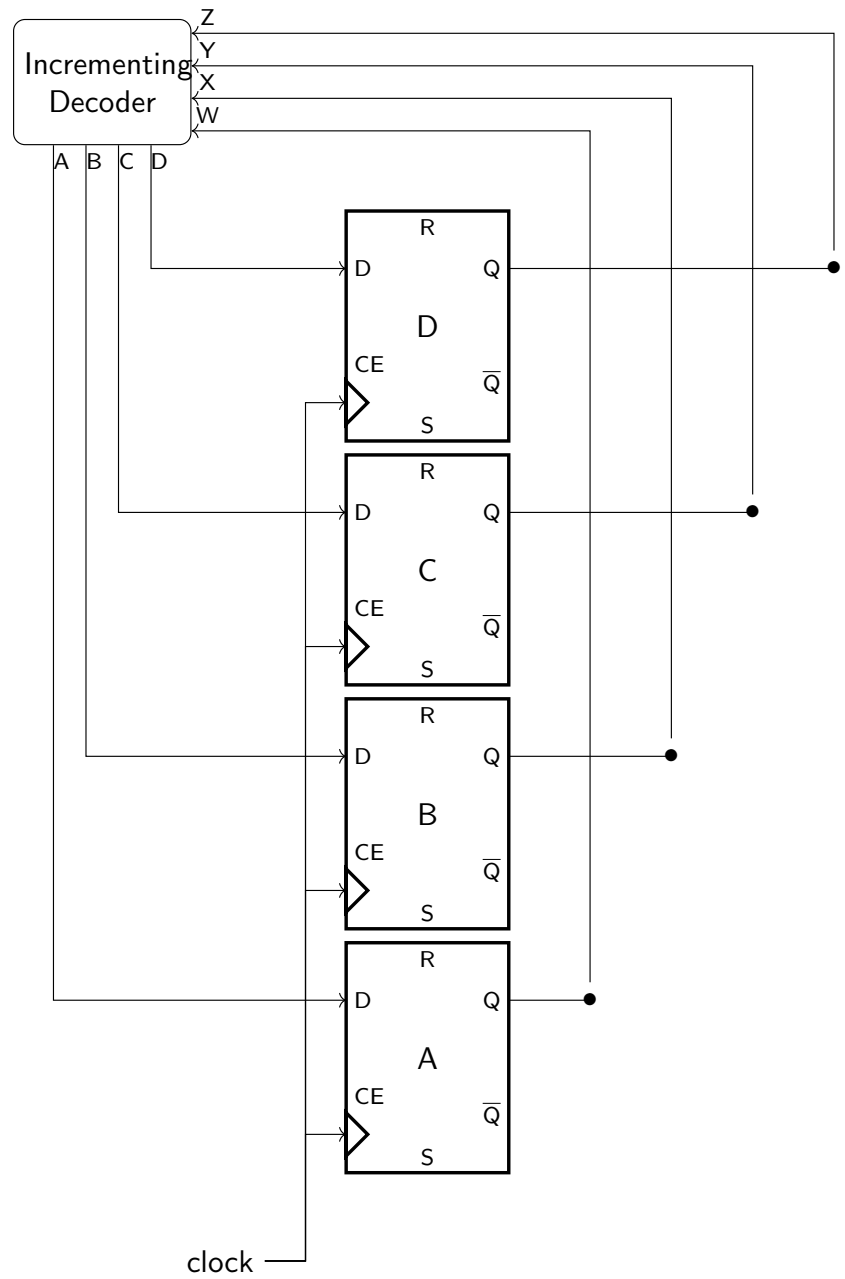


Figure 6.2: Decade counter FSM implementation using D-Flip Flops

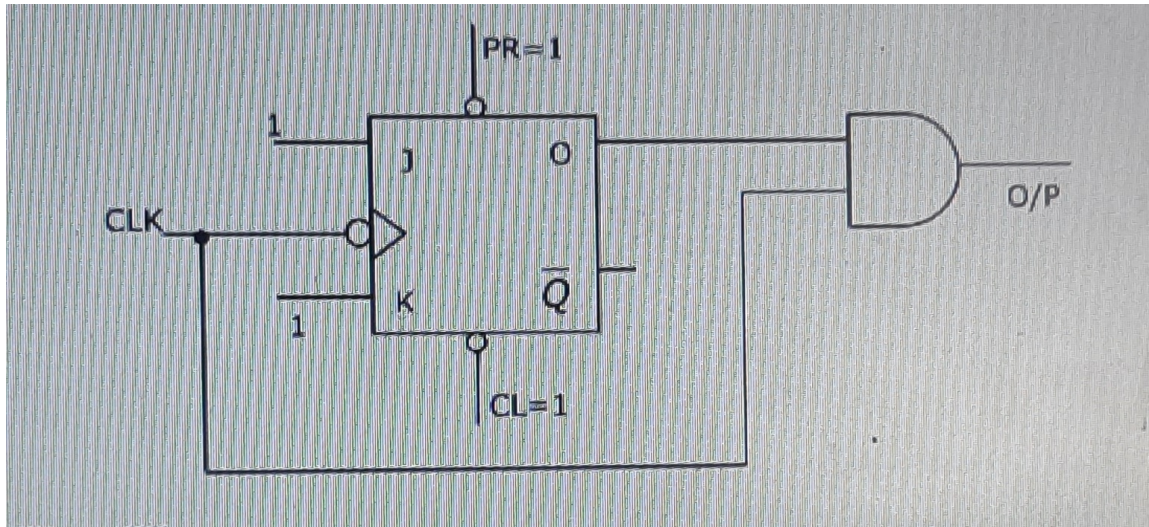


Figure 6.3:

2. The circuit shown in the figure below uses ideal positive edge-triggered synchronous J-K flip flops with outputs X and Y. If the initial state of the output is $X=0$ and $Y=0$, just before the arrival of the first clock pulse, the state of the output just before the arrival of the second clock pulse is (GATE IN 2019)

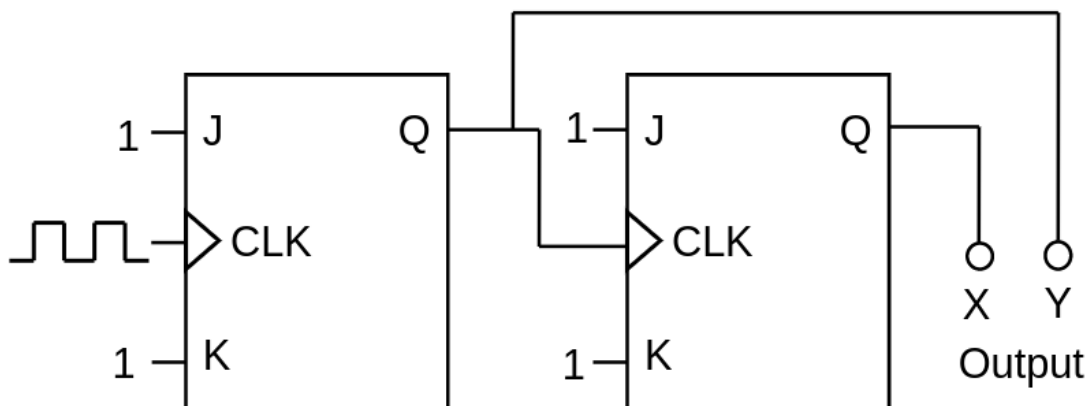


Figure 6.4:

3. The state diagram of a sequence detector is shown in Fig. 6.5 . State S_0 is the initial state of the sequence detector. If the output is 1, then (GATE EC 2020)

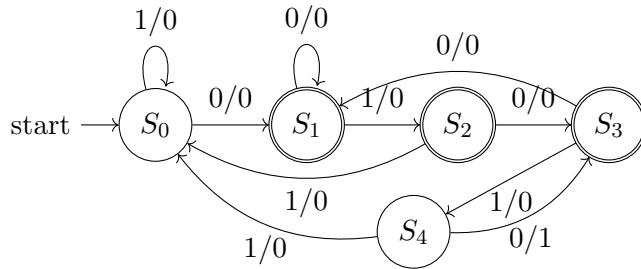


Figure 6.5: State diagram

- (a) the sequence 01010 is detected
- (b) the sequence 01011 is detected
- (c) the sequence 01110 is detected
- (d) the sequence 01001 is detected
4. A counter is constructed with three D flip-flops. The input-output pairs are named (D0, Q0), (D1, Q1), and (D2, Q2), where the subscript 0 denotes the least significant bit. The output sequence is desired to be the Gray-code sequence 000, 001, 011, 010, 110, 111, 101, and 100, repeating periodically. Note that the bits are listed in the Q2 Q1 Q0 format. Find the combinational logic expression for D1. (GATE EE 2021)
5. For the circuit shown in Fig. 6.6, the clock frequency is f_0 and the duty cycle is 25%. For the signal at the Q output of the Flip-Flop,
- (a) frequency of $\frac{f_0}{4}$ and duty cycle is 50%
- (b) frequency of $\frac{f_0}{4}$ and duty cycle is 25%
- (c) frequency of $\frac{f_0}{2}$ and duty cycle is 50%

(d) frequency of f_0 and duty cycle is 25%

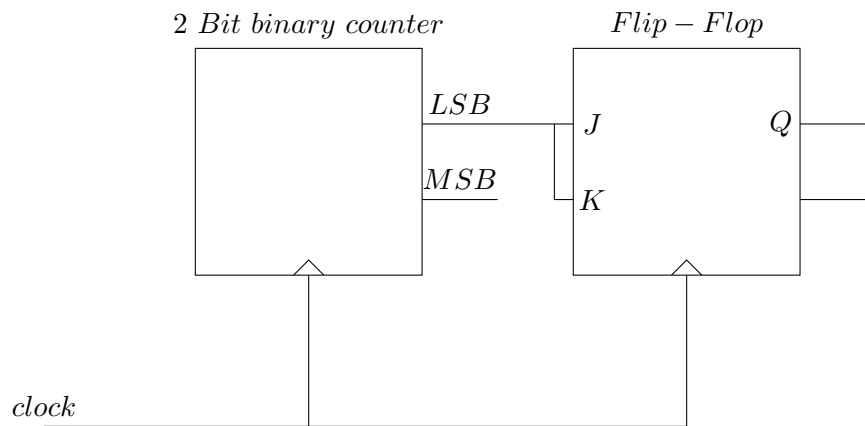


Figure 6.6:

(GATE EC-2022)

6. A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequences detectable. For the sequence (1, 0, 1) and input data (1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0), what is the output of this detector?

- (a) 1,1,0,0,0,0,1,1,0,1,0,0
- (b) 0,1,0,0,0,0,0,1,0,1,0,0
- (c) 0,1,0,0,0,0,0,1,0,1,1,0
- (d) 0,1,0,0,0,0,0,0,1,0,0,0

(GATE EE 2020)

7. Two T-flip flops are interconnected as shown in Fig. 6.7. The present state of the flip flops are: $A = 1, B = 1$. The input x is given as 1, 0, 1 in the next three clock cycles.

The decimal equivalent of $(ABy)_2$ with A being the MSB and y being the LSB, after the 3rd clock cycle is _____

 


Figure 6.7:

(GATE IN 2020)

8. In the circuit shown below, a positive edge-triggered D flip-flop is used for sampling input data using clock CK. The XOR gate outputs 3.3 volts for logic HIGH and 0 volts for logic LOW levels. The data bit and clock periods are equal and the value of $\Delta T/T_{ck} = 0.15$, where the parameters ΔT and T_{ck} are shown in the figure. Assume that the Flip and the XOR gate are ideal. (GATE EC 2018)

9. A 2-bit synchronous counter using two J-K flip flops is shown. The expressions for the inputs to the J-K flip flops are also shown in the figure. The output sequence of the counter starting from $Q_1Q_2 = 00$ is

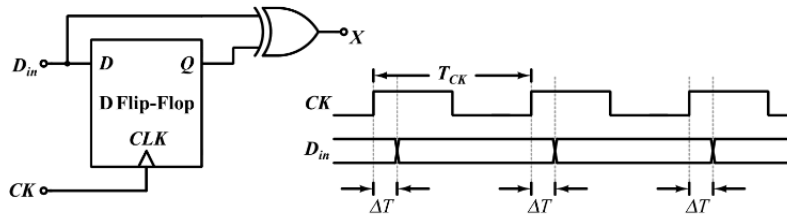


Figure 6.8: image

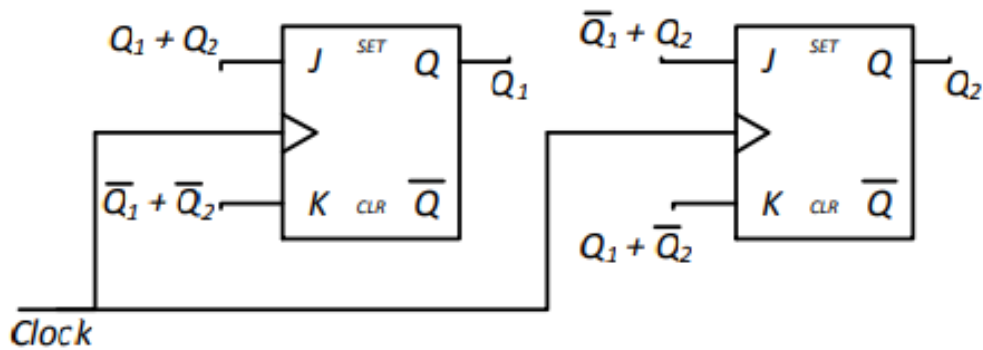


Figure 6.9: 2-bit synchronous counter

- (a) $00 \rightarrow 11 \rightarrow 10 \rightarrow 01 \rightarrow 00 \dots$
- (b) $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \dots$
- (c) $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \dots$
- (d) $00 \rightarrow 10 \rightarrow 11 \rightarrow 01 \rightarrow 00 \dots$

GATE IN 2018

10. Let p and q be two propositions. Consider the following two formulae in propositional

logic.

$$S_1 : (\neg p \vee (p \wedge q)) \rightarrow q \quad (6.2)$$

$$S_2 : q \rightarrow (\neg p \vee (p \wedge q)) \quad (6.3)$$

Which one of the following choices is correct? (GATE-CS2021)

- (A) Both S_1 and S_2 are tautologies.
- (B) S_1 is a tautology but S_2 is not a tautology.
- (C) S_1 is not a tautology but S_2 is a tautology.
- (D) Neither S_1 nor S_2 is a tautology.

11. Consider a 3-bit counter, designed using T flip-flops, as shown below:

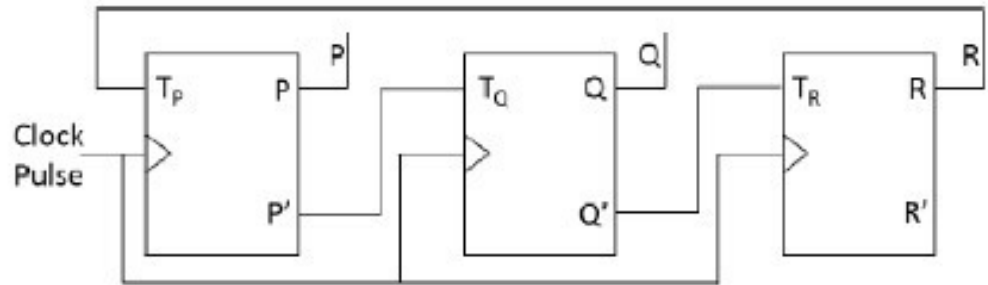


Figure 6.10:

Assuming the initial state of the counter given by PQR as 000, what are the next three states? (GATE-CS2021)

- (A) 011, 101, 000
- (B) 010, 101, 000
- (C) 010, 101, 000

(D) 010,101,000

12. The state diagram of a sequence detector is shown below. state S_0 is the initial state of the sequence detector. If the output is 1, then (GATE-EC2020,39)

 


Figure 6.11: State diagram of a sequence detector

- (a) the sequence 01010 is detected.
- (b) the sequence 01011 is detected.
- (c) the sequence 01110 is detected.
- (d) the sequence 01001 is detected.

13. The state transition diagram for the circuit shown is (GATE-IN2019,39)



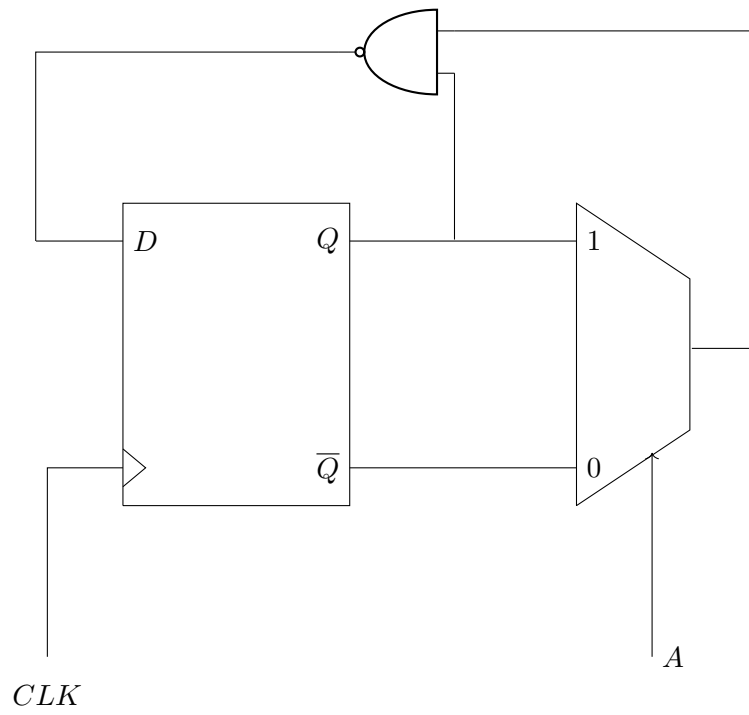



Figure 6.12: Circuit Diagram

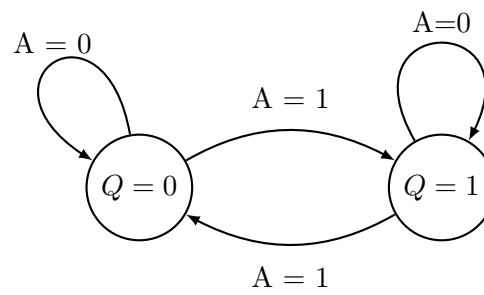


(a)

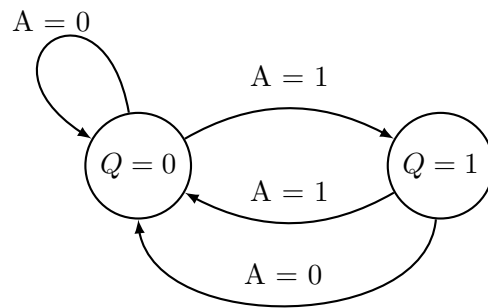

(b)

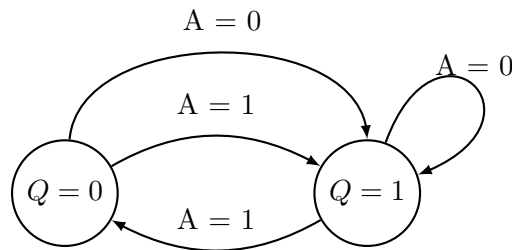

(c)

 

(d)

14. An 8085 microprocessor accesses two memory locations (2001H) and (2002H), that contain 8-bit numbers 98H and B1H, respectively. The following program is executed:

```

LXI H,2001H
MVI A,21H
INX H
ADD M
INX H
MOV M,A
HLT

```

At the end of this program, the memory location 2003H contains the number in decimal (*base10*) form _____.

(*GATE EE2020 – 54*)

15. A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequences detectable. For the sequence (1, 0, 1) and input data (1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0).
(*GATE EE2020 – 15*)

- (a) (1, 1, 0, 0, 0, 0, 1, 1, 0, 1, 0, 0)
- (b) (0, 1, 0, 0, 0, 0, 0, 1, 0, 1, 0, 0)
- (c) (0, 1, 0, 0, 0, 0, 0, 1, 0, 1, 1, 0)
- (d) (0, 1, 0, 0, 0, 0, 0, 0, 1, 0, 0, 0)

16. A 16-bit synchronous binary up-counter is clocked with the frequency f_{CLK} . The two most significant bits are **OR**-ed together to form an output Y . Measurements show that Y is periodic, and the duration for which Y remains high in each period is 24 ms. The clock frequency _____ MHz.

(Round off to 2 decimal places.)

(*GATE EE2021 – 22*)

17. which of the following is the correct binary equivalent of the hexadecimal F6C?

(GATE PH2020,6)

(a) 011011111100

(b) 111101101100

(c) 110001101111

(d) 011011000111

18. P, Q, and R are the decimal integers corresponding to the 4-bit binary number 1100 consider in single magnitude, 1's complement, and 2's complement representations, respectively. The 6-bit 2's complement representation of $(P + Q + R)$ is

(GATE EC-2020,38)

(a) 110101

(b) 110010

(c) 111101

(d) 111001