

Implementation of Boolean Logic in Arduino using IC 7474

Sai Harshith Kalithkar
harshith.work@gmail.com
FWC22118

IIT Hyderabad-Future Wireless Communication Assignment

February 2023

Contents

1 Problem

2

1 Problem

(GATE EC-2022)

Q.43. For the circuit shown, the clock frequency is f_0 and the duty cycle is 25%.
For the signal at the Q output of the Flip-Flop,

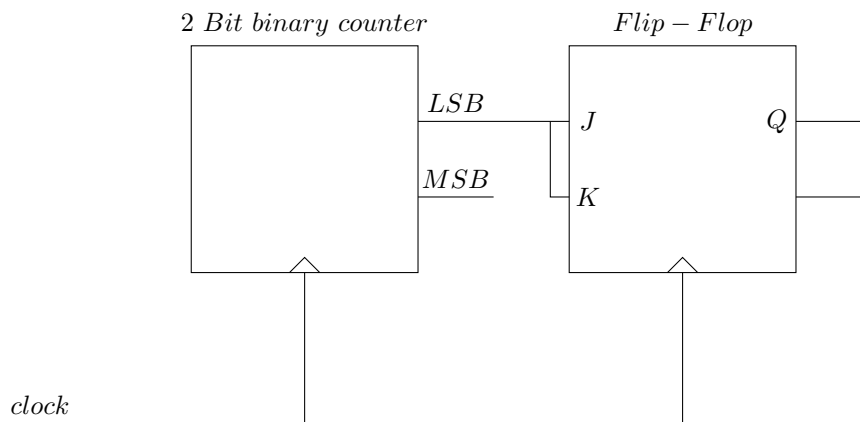


Figure 1: Diagram

1. frequency of $\frac{f_0}{4}$ and duty cycle is 50%

2. frequency of $\frac{f_0}{4}$ and duty cycle is 25%
3. frequency of $\frac{f_0}{2}$ and duty cycle is 50%
4. frequency of f_0 and duty cycle is 25%